

Question **1**
Complete
Mark 1.00 out of 1.00

Flag question

Question text

Wire ends in a metal-tipped wand called circuits.

Select one:

True

False

Question **2**
Complete
Mark 1.00 out of 1.00

Flag question

Question text

The unit of Power is WATT(W).

Select one:

True

False

Question **3**
Complete
Mark 1.00 out of 1.00

Flag question

Question text

Voltmeter is connected in parallel with a device to measure it's voltage.

Select one:

True



False

Question **4**

Complete

Mark 1.00 out of 1.00

Flag question

Question text

Ammeter and Voltmeter are considered device used in a circuit.

Select one:



True



False

Question **5**

Complete

Mark 1.00 out of 1.00

Flag question

Question text

Ammeter is used to measure Current.

Select one:



True



False

Question **6**

Complete

Mark 1.00 out of 1.00

Flag question

Question text

A voltmeter is connected Series in a resistors to measure voltage.

Select one:

True

False

Question **7**

Complete

Mark 1.00 out of 1.00

Flag question

Question text

The unit of current is OHM.

Select one:

True

False

Question **8**

Complete

Mark 1.00 out of 1.00

Flag question

Question text

Ammeter is connected in series with a device to measure it's voltage.

Select one:

True

False

Question **9**

Complete

Mark 1.00 out of 1.00

Flag question

Question text

A circuit cannot functions without a source.

Select one:

True

False

Question **10**

Complete

Mark 1.00 out of 1.00

Flag question

Question text

Resistivity is a measure of the resistance of a given size of a specific material to electrical conduction.

Select one:

True

False

Question **11**

Complete

Mark 1.00 out of 1.00

Flag question

Question text

A voltmeter is consist of a box with two wires a positive and a negative.

Select one:

True

False

Question **12**

Complete

Mark 1.00 out of 1.00

Flag question

Question text

Ammeter is used to measure Voltage.

Select one:

True

False

Question **13**

Complete

Mark 1.00 out of 1.00

Flag question

Question text

Energy is a rate at which work is done and it is the rate at which Energy transferred.

Select one:

True

False

Question **14**

Complete

Mark 1.00 out of 1.00

Flag question

Question text

Ammeter is connected in parallel with a device to measure it's current.

Select one:

True

False

Question **15**
Complete
Mark 1.00 out of 1.00

Flag question

Question text

The unit of Volts is called Voltmeter.

Select one:

True

False

Question **16**
Complete
Mark 1.00 out of 1.00

Flag question

Question text

Current is measured in Amperes.

Select one:

True

False

Question **17**
Complete
Mark 1.00 out of 1.00

Flag question

Question text

Symbol 'A' stands for length of ammeter.

Select one:

True

False

Question **18**
Complete
Mark 1.00 out of 1.00

Flag question

Question text

Voltmeter is a device used for measuring the potential difference between 2 different points in space.

Select one:

True

False

Question **19**
Complete
Mark 1.00 out of 1.00

Flag question

Question text

Ammeter and Voltmeter that measures charges.

Select one:

True

False

Question **20**
Complete
Mark 1.00 out of 1.00

Flag question

Question text

Ammeter is connected parallel in a device.

Select one:



True



False