
Dc motors

1. A 20hp, 250V shunt motor with $R_a=0.22 \Omega$, $R_f=170 \Omega$. At no-load and rated voltage, the speed is 1200 rpm and the armature current is 3 A. At full-load and rated voltage, the line current is 55A. What is the full-load speed?

Solution

At No-load

$$I_{f\ n.l} = \frac{V_t}{R_f} = \frac{250}{170} = 1.47\ A ,$$

$$N_{n.l} = 1200\ r.p.m$$

$$E_{n.l} = V_t - I_a R_a = 250 - (3)(0.22) = 249.34\ V$$

At Full-load

$$I_{f\ f.l} = \frac{V_t}{R_f} = \frac{250}{170} = 1.47\ A , N_{f.l} = ??$$

$$E_{f.l} = V_t - I_a R_a = 250 - (55)(0.22) = 238.22\ V$$

$$\frac{E_{n.l}}{E_{f.l}} = \frac{I_{f\ n.l} N_{n.l}}{I_{f\ f.l} N_{f.l}}$$

$$\frac{249.34}{238.22} = \frac{1200}{N_{f.l}}$$

$$N_{f.l} = 1146.5\ r.p.m$$

2. A separately excited motor runs at 1045rpm, with a constant field current, while taking an armature current of 50A at 120V. The armature resistance is 0.1Ω if the load on the motor changes such that it now takes 95A at 120V, determine the motor speed at this load.

Solution

$$E = K_a \phi \omega = K \phi N$$

$$\frac{E_1}{E_2} = \frac{\phi_1 N_1}{\phi_2 N_2}$$

\therefore the field current is constant and the core is assumed unsaturated

$$\therefore \phi_1 = \phi_2$$

$$\therefore \frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$E = V_t - I_a R_a$$

$$E_1 = 120 - (50)(0.1) = 115 \text{ V}$$

$$E_2 = 120 - (95)(0.1) = 110.5 \text{ V}$$

$$\frac{115}{110.5} = \frac{1045}{N_2}$$

$$N_2 = 1004.1 \text{ r.p.m}$$

3. A separately excited DC motor has the following specifications:
Terminal voltage = 250 V, field voltage = 250 V, armature resistance = 0.03 Ω , field resistance = 250 Ω . Initially the motor was running at speed = 1103 rpm while supplied by the rated terminal voltage and the armature current = 120 A. While supplying constant torque, what is the speed of the motor if the terminal voltage is reduced to 200 V?

Torque is constant and V_f is not changed (the field flux will be constant)

$$T = K_a \phi I_a$$

$$T_1 = T_2$$

$$\phi_1 I_{a1} = \phi_2 I_{a2}$$

$$I_{a1} = I_{a2} = 120 \text{ A}$$

$$E = K_a \phi \omega = K \phi N$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$E_1 = V_{t1} - I_{a1} R_a = 250 - (120)(0.03) = 246.4 \text{ V}$$

$$E_2 = V_{t2} - I_{a2} R_a = 200 - (120)(0.03) = 196.4 \text{ V}$$

$$N_2 = \frac{E_2}{E_1} N_1$$

$$= \frac{196.4}{246.4} * 1103$$

$$= 879.5 \text{ r.p.m}$$

4. A 20 hp, 250 V DC shunt motor drives a load that requires a constant torque regardless the speed of operation. The armature resistance is 0.1Ω . When this motor is running at full load, the armature current is 65 A at a speed of 1100 rpm. If the flux is reduced to 75% of its original value, find the armature current and the speed of the motor at this new condition?

Solution

Torque is constant

$$T_1 = T_2$$

$$\phi_1 I_{a1} = \phi_2 I_{a2}$$

$$\phi_1 I_{a1} = 0.75 \phi_1 I_{a2}$$

$$I_{a1} = 0.75 I_{a2}$$

$$65 = 0.75 I_{a2}$$

$$I_{a2} = 86.6 \text{ A}$$

$$E = K_a \phi \omega = K \phi N$$

$$\frac{E_1}{E_2} = \frac{\phi_1 N_1}{\phi_2 N_2} = \frac{\phi_1 N_1}{0.75 \phi_1 N_2} = \frac{1 N_1}{0.75 N_2}$$

$$E = V_t - I_a R_a$$

$$E_1 = V_{t1} - I_{a1} R_a = 250 - (65)(0.1) = 243.5 \text{ V}$$

$$E_2 = V_{t2} - I_{a2} R_a = 250 - (86.6)(0.1) = 241.4 \text{ V}$$

$$\frac{243.5}{241.4} = \frac{1 N_1}{0.75 N_2}$$

$$N_2 = 1454 \text{ r.p.m}$$