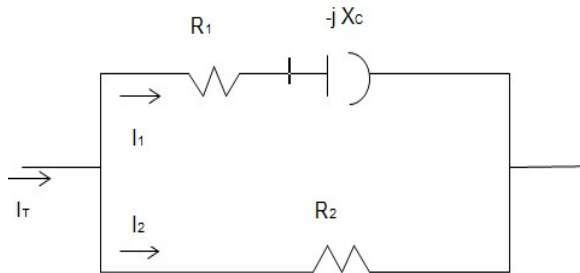


Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

BERNABE,DAVE REYNOLD  
CLEMENTE,SHANE CARLYNE  
CLERIGO,JENICA  
DEOMAMPO, LYXANDER  
PAPIO,RAY JOHN  
SIMAN,ANN LORRAINE  
YUZON,RUEL

1) In the circuit shown below, the total effective current is 30 amperes. Determine the power relations.



Given:  $R_1 = 5\ \Omega$ ;  $R_2 = 4\ \Omega$ ;  $-jX_1 = -j3\ \Omega$ ;  $I_T = 30\ \angle 0^\circ\ \text{A}$

Solution:

$$I_2 = (30\ \angle 0^\circ) [(5-j3)] \div [(9-j3)] = 18.45\ \angle -12.55^\circ\ \text{A}$$

$$I_1 = (30\ \angle 0^\circ) [(4) \div (9-j3)] = 12.7\ \angle 18.45^\circ\ \text{A}$$

$$P = I_2^2 R_2 + I_1^2 R_1$$

$$P = (18.45)^2(4) + (12.7)^2(5)$$

$$P = 2165\ \text{W}$$

$$Q = I_1^2 X_1$$

$$Q = (12.7)^2(3)$$

$$Q = 483\ \text{VAR (Leading)}$$

$$S = P - jQ$$

$$S = 2165 - j483$$



$$S = 2210\ \angle -12.6^\circ$$

$$\text{P.f.} = P / S$$

$$\text{P.f.} = 2165 / 2210$$

$$\text{P.f.} = 0.98\ \text{Leading}$$

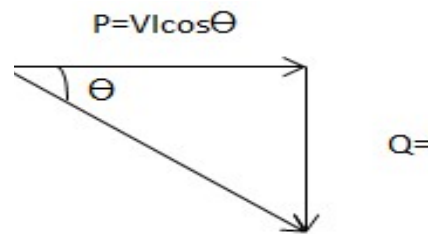 2) A two circuit element is connected in a series;  $R=5\Omega$  and  $X_L= 15\Omega$  has an effective voltage across the resistor of 31.6V. Determine the power triangle



Solution:

$$I = V_R / R$$

$$I = 31.6 / 5$$

$$I = 6.32 \text{ A}$$

$$Z_L = R + jX_L$$

$$Z_L = 5 + j15$$

$$Z_L = 15.81 \angle 71.56^\circ$$

$$\tan \theta = X_L / R = 15/5$$

$$\theta = \tan^{-1}(3)$$

$$\theta = 71.56^\circ$$

$$\text{Apparent Power} = VI = I^2Z = (6.32)^2(15.81 \angle 71.56^\circ)$$

$$S = 631.48 \angle 71.56^\circ \text{ VA}$$

$$S = 200 + j600 \text{ VA}$$

$$\text{Reactive Power} = I^2X_L = (6.32)^2(15)$$

$$Q = 600 \text{ VAR Lagging}$$

$$\text{Real Power} = I^2R = (6.32)^2(5)$$

$$P = 200 \text{ Watts}$$


Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

 3) A series circuit of  $R = 8\Omega$  and  $X_C=6\Omega$  has an applied phasor voltage  $V = 50\angle -90^\circ$ . Find the complete phasor information.



Given:  $R= 8\Omega$ ;  $X_C= 6\Omega$ ;  $V=50\angle -90^\circ$

Solution:

$$Z_C = R - j X_C$$

$$Z_C = 8 - j6$$

$$Z_C = 10\angle -36.86^\circ$$

$$I = V / Z_C$$

$$I = (50\angle -90^\circ) / (10\angle -36.86^\circ)$$

$$I = 5\angle -53.13^\circ \text{ A}$$

$$S = I^2 Z$$

$$S = (5\angle -53.13^\circ)^2 (10\angle -36.86^\circ)$$

$$S = 250\angle -143.14^\circ \text{ VA}$$

$$S = -200 - j150 \text{ VA}$$

$$P = I^2 R$$

$$P = (5)^2 (8)$$

$$P = 200 \text{ W}$$

$$Q = I^2 X_C$$

$$Q = (5)^2 (6)$$


$$Q = 150 \text{ VAR}$$

$$\text{P.f.} = \cos \theta$$

$$\text{P.f.} = \cos 36.86^\circ$$

$$\text{P.f.} = 0.8 \text{ Leading}$$

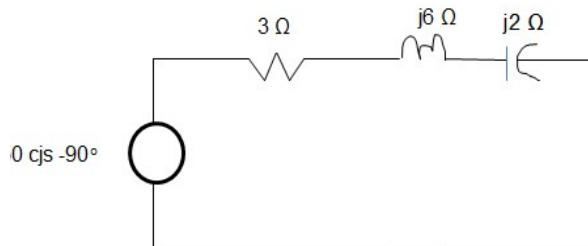4) Given the series circuit of figure below, determine the power triangle.



Solution:

$$\begin{aligned} \text{From the figure } Z &= (3 + j6 - j2) \Omega \\ &= 3 + j4 \Omega \\ &= 5 \angle 53.1^\circ \end{aligned}$$

$$I = V/Z$$

$$I = (50 \angle -90^\circ) / (5 \angle 53.1^\circ)$$

$$I = 10 \angle -143.1^\circ \text{ A}$$

$$S = VI$$

$$S = (50 \angle -90^\circ) (10 \angle -143.1^\circ)$$

$$S = 500 \angle 53.1^\circ \text{ VA}$$

$$S = 300 + j400 \text{ VA}$$

Therefore the components are:

$$P = 300 \text{ W}$$

$$Q = 400 \text{ VAR Lagging}$$

$$S = 500 \text{ VA}$$

$$\text{P.f} = \cos 53.1^\circ = 0.6 \text{ Lagging}$$


Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

 5) Determine the power triangles for each branch the parallel circuit and add them to obtain the power triangle for the entire circuit.



Given:  $Z_1 = 4 \angle 30^\circ \Omega$  ;  $Z_2 = 5 \angle 60^\circ \Omega$

Solution:

For branch 1

$$I_1 = V/Z_1$$

$$I_1 = (20 \angle 60^\circ) / (4 \angle 30^\circ)$$

$$I_1 = 5 \angle 30^\circ \text{ A}$$

$$S_1 = VI_1$$

$$S_1 = (20 \angle 60^\circ) / (5 \angle -30^\circ)$$

$$S_1 = 100 \angle 30^\circ \text{ VA}$$

$$S_1 = 86.6 + j50 \text{ VA}$$

Then;  $P_1 = 86.6 \text{ W}$  ;  $Q_1 = 50 \text{ VAR Lagging}$  ;  $S_1 = 100 \text{ VA}$  ;  $P.F = 0.866$

For branch 2

$$I_2 = V/Z_2$$

$$I_2 = (20 \angle 60^\circ) / (5 \angle 60^\circ)$$

$$I_2 = 4 \angle 0^\circ \text{ A}$$

$$S_2 = VI_2$$

$$S_2 = (20 \angle 60^\circ) / (4 \angle 0^\circ)$$

$$S_2 = 80 \angle 60^\circ \text{ VA}$$

$$S_2 = 40 + j69.2 \text{ VA}$$

Then;  $P_2 = 40 \text{ W}$  ;  $Q_2 = 69.2 \text{ VAR Lagging}$  ;  $S_2 = 80 \text{ VA}$  ;  $P.F = 0.5$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

Therefore;

$$P_T = P_1 + P_2$$

$$P_T = 86.6 \text{ W} + 40 \text{ W}$$

$$P_T = 126.6 \text{ W}$$

$$Q_T = Q_1 + Q_2$$

$$Q_T = 50 \text{ VAR} + 69.2 \text{ VAR}$$

$$Q_T = 119.2 \text{ VAR (Lagging)}$$

$$S_T = P_T + jQ_T$$

$$S_T = 126.6 + j119.2$$

$$S_T = 174.0 \angle 43.4^\circ \text{ VA}$$

$$P.F._T = P_T / S_T$$

$$P.F._T = 126.6 / 174$$

$$P.F._T = 0.727 \text{ Lagging}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

6) An induction motor with a 2HP output has an efficiency of 85%. At this load the power factor is 0.8 lagging. Determine the complete input power information,

Given:  $P_o = 2\text{HP}$  ;  $\text{Eff.} = 85\%$

Solution:

$$P_{IN} = P_o / \text{Eff}$$

$$P_{IN} = [(2\text{Hp})(746 \text{ Watts} / 1 \text{ Hp})] / 0.85$$

$$P_{IN} = 1755 \text{ Watts}$$

$$\cos \theta = 0.8$$

$$\theta = \cos^{-1} 0.8$$

$$\theta = 36.9^\circ$$

$$\cos \theta = P/S ; S = P/\cos \theta$$

Therefore;

$$S = 1755 / 0.8$$

$$S = 2190 \text{ VA}$$

$$\cos \theta = Q/S$$

$$Q = 2190 \sin 36.9^\circ$$

$$Q = 1315 \text{ VAR}$$

7) Determine the total power triangle for the parallel circuit of figure below if the power in the  $2\Omega$  resistor is 20 Watts.

Given:

$$P_1 = 20 \text{ Watts}$$

$$Z_1 = 2 - j5 \Omega = 5.38 \angle -68.2^\circ$$

$$Z_2 = 1 + j1 \Omega$$

Solution:

$$P = I_1^2 R_1$$

$$I_1 = \sqrt{\frac{P}{R}}$$

$$I_1 = \sqrt{\frac{20}{2}}$$

$$I_1 = 3.16 \text{ A}$$

$$V = I_1 Z_1$$

$$V = (3.16)(5.38)$$

$$V = 17 \text{ Volts}$$

Let  $V = 17 \angle 0^\circ$  then,

$$I_1 = 3.16 \angle 68.2^\circ \text{ A}$$

$$I_2 = (17 \angle 0^\circ) / (\sqrt{2} \angle 45^\circ)$$

$$I_2 = 12 \angle -45^\circ \text{ A}$$

$$I_T = I_1 + I_2$$

$$I_T = 3.16 \angle 68.2^\circ + 12 \angle -45^\circ$$

$$I_T = 11.1 \angle -29.8^\circ \text{ A}$$

$$S_T = VI_T$$

$$S_T = (17 \angle 0^\circ)(11.1 \angle -29.8^\circ)$$

$$S_T = 189 \angle -29.8^\circ \text{ VA}$$

$$S_T = 164 + j94 \text{ VA}$$

$$\text{P.F.} = 164/189 = 0.868 \text{ Lagging}$$

8) Determine the power component of a combination of the three individual loads specified as follows: load 1: 250 VA, p.f.= 0.5 lagging; Load2: 180W, p.f.=0.8 leading; Load3: 300 VA, 100 VAR lagging. Calculate the unknown average power and reactive power of each load.

Given:

Load 1 : 250 VA , p.f = 0.5 leading

Load 2 : 180 W , p.f = 0.8 leading

Load 3 : 300 VA , 100 VAR lagging

Solution:

For Load 1,

$$\cos \theta = 0.5$$

$$\theta = \cos^{-1} 0.5$$

$$\theta = 60^\circ$$

$$P = S \cos \theta$$

$$P = (250)(0.5)$$

$$P = 125 \text{ W}$$

$$Q = S \sin \theta$$

$$Q = (250)(\sin 60)$$

$$Q = 216 \text{ VAR}$$

For Load 2,

$$\cos \theta = 0.8$$

$$\theta = \cos^{-1} 0.8$$

$$\theta = 36.9^\circ$$

$$S = P / \cos \theta$$

$$S = (180) / (0.8)$$

$$S = 225 \text{ VA}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

For Load 3,

$$\theta = \sin^{-1} (Q / S)$$

$$\theta = \sin^{-1} (100 / 300)$$

$$\theta = 19.5^\circ$$

$$P = S \cos \theta$$

$$P = (300)(\cos 19.5^\circ)$$

$$P = 283 \text{ W}$$

Therefore,

$$P_T = P_1 + P_2 + P_3$$

$$P_T = 125 + 180 + 283$$

$$P_T = 588 \text{ Watts}$$

$$Q_T = Q_1 + Q_2 + Q_3$$

$$Q_T = 216 + (-135) + 100$$

$$Q_T = 181 \text{ VAR Lagging}$$

Since  $S_T = P_{ST} + j Q_{ST}$

Therefore,

$$S_T = 588 + j181$$

$$S_T = 616 \angle 17.1^\circ \text{ VA}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

9) A two element series circuit with an instantaneous current  $i = 4.24 \sin (5000t + 45^\circ)$ . Has a power of 180 Watts and a power factor of 0.8 lagging. Find the circuit constants.

Given:

$$i = 4.24 \sin (5000t + 45^\circ) \text{ A}$$

$$P = 180 \text{ W}$$

$$\cos \theta = 0.8$$

Solution:

$$\text{The effective value of current} = (4.24) / \sqrt{2} = 3.0 \text{ A}$$

$$P = I^2 R$$

$$R = (180) / (3)^2$$

$$\text{Impedance angle } \theta = \cos^{-1} 0.8 = 36.87^\circ$$

Number 2 element is an inductor, using power triangle,

$$(Q / P) = \tan 36.87^\circ = [(I_{\text{eff}})^2 (X_L)] / 180$$

$$X_L = (180 \tan 36.87^\circ) / 3^2$$

$$X_L = 15.0 \Omega$$

Since  $X_L = 2 \pi f L$

$$\omega = 2 \pi f = 5000$$

$$15 = 5000L$$

$$L = 15 / 5000$$

$$L = 3 \text{ mH}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

10) Two impedances  $Z_1=5.83 \angle -59^\circ \Omega$  and  $Z_2= 8.95 \angle 63.4^\circ$  are in series and pass an effective current of a 5 amp. Determine the complete power information.

Given:  $Z_1=5.83 \angle -59^\circ \Omega$  ;  $Z_2= 8.95 \angle 63.4^\circ$

Solution:

For series impedances;  $Z_T=Z_1 + Z_2$

$$Z_T = (5.83 \angle -59^\circ) + (8.95 \angle 63.4^\circ)$$

$$Z_T = 7.0 + j 3 \Omega$$

$$P_T = I^2 R$$

$$P_T = (5)^2(7)$$

$$P_T = 175W$$

$$Q_T = I^2 X_L$$

$$Q_T = (5)^2(3)$$

$$Q_T = 75VAR$$

$$S_T = \sqrt{P_T^2 + Q_T^2}$$

$$S_T = \sqrt{(175)^2 + (75)^2}$$

$$S_T = 190.4 VA$$

$$P.f = P_T / S_T$$

$$P.f = 175 / 190.4$$

$$P.f = 0.918 \text{ lagging}$$

11) A 500 kVA transformer is at full load with an overall power factor of 0.6 lagging. The power factor is improved by adding capacitors until the overall power factor becomes 0.9 lagging. Determine the kVAR of capacitors required after correction of the power factor, what percentage of full load is the transformer carrying?

Solution:

$$\cos \theta = P/S ; S= 500VA$$

$$P= 500 \cos \theta$$

$$P= 500 (0.6)$$

$$P= 300 kW$$

$$\theta = \cos^{-1} 0.6$$

$$\theta = 53.1^\circ$$

$$Q= V \sin \theta$$

$$Q=500 \sin 53.1^\circ$$

$$Q= 400 \text{ kVAR lagging}$$

When

$$\cos \theta = 0.9 \text{ lagging,}$$

$$\theta = \cos^{-1} 0.9$$

$$\theta = 26^\circ$$

$$S' = 300 / 0.9$$

$$S' = 333 \text{ kVA}$$

$$Q' = 333 \sin 26^\circ$$


$$Q' = 146 \text{ kVAR}$$

$$\text{Capacitor kVAR} = Q - Q' = 400 - 146$$

$$Q = 254 \text{ leading}$$

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

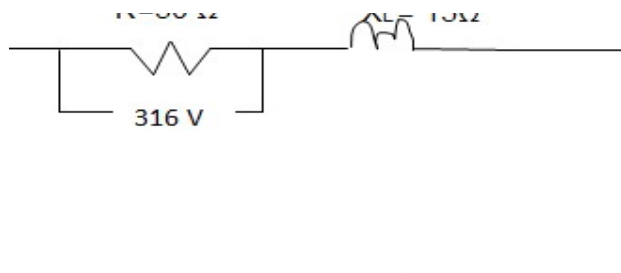12) A two-element series circuit with  $R = 5 \Omega$  and  $X_L = 15 \Omega$  has an effective voltage of 31.6 volt across the resistor. Find the complex power and the power factor.



Given:

$$R = 5 \Omega$$

$$X_L = 15 \Omega$$

$$E_R = 31.6 \text{ V}$$

Solution:

$$I = V_R / R$$

$$I = 31.6 / 5$$

$$I = 6.32 \text{ A}$$

$$P_R = I^2 R$$

$$P_R = (6.32)^2 (5)$$

$$P_R = 200 \text{ W}$$

$$Q_L = I^2 X_L$$

$$Q_L = (6.32)^2 (15)$$

$$Q_L = 600 \text{ VARS}$$

$$\text{Complex Power} = 200 + j 600$$

$$\text{Power Factor} = P / S$$

$$\text{Power Factor} = 200 / \sqrt{(200)^2 + (600)^2}$$

$$\text{Power Factor} = 0.316 \text{ lagging}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

13) A circuit with impedance  $z=8-j6 \Omega$  has an applied phasor voltage  $V= 70.7 \angle -90^\circ$ . Obtain the power triangle.

Given:

$$Z= 8-j6 \Omega$$

$$V= 70.7 \angle -90^\circ \text{ V}$$

Solution:

$$Z= 8-j6$$

$$Z= R- j X_c$$

$$\text{Effective Voltage} = (\text{Phase Voltage}) / \sqrt{2} = (70.7) / \sqrt{2}$$
$$= 50 \text{ V}$$

$$I_{\text{effective}} = 50 / 10 = 5 \text{ A}$$

$$P= I^2R$$

$$P= (5)^2(8)$$

$$P= 200 \text{ Watts}$$

$$Q_c= I^2X_c$$

$$Q_c= (5)^2(6)$$

$$Q_c=150 \text{ VAR}$$

$$\text{P.f.} = P/S$$

$$\text{P.f.} = 200 / \sqrt{(200)^2 + (150)^2}$$

$$\text{P.f.} = 0.8 \text{ leading}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

14) Determine the circuit impedance which has a complex power of  $S = 5031 \angle -26.57^\circ$  for an applied phasor voltage  $212.1 \angle 0^\circ$  V.

Given:

$$S = 5031 \angle -26.57^\circ$$

$$V = 212.1 \angle 0^\circ \text{ V}$$

Solution:

$$\text{Effective Voltage} = (212.2) / \sqrt{2} = 150 \text{ V}$$

$$S = 4500 - j2250$$

$$P = 4500 \text{ W}$$

$$Q_c = 2250 \text{ VAR}$$

$$\text{P.f} = 4500 / 5031$$

$$\text{P.f} = 0.894 \text{ Leading}$$

$$P = EI \cos \theta$$

$$I = 4500 / (150)(0.894)$$

$$I = 33.55 \text{ A}$$

$$P = I^2 R$$

$$R = 4500 / (33.55)^2$$

$$R = 4 \Omega$$

$$Q_c = I^2 X_c$$

$$X_c = 2250 / (33.55)^2$$

$$X_c = 2.0 \Omega$$

$$Z = R - jX_c$$

$$Z = 4 - j 2 \Omega$$

15) Determine the impedance corresponding to apparent power 3,500 VA, power factor of 0.76 lagging and effective current of 18.0A.

Given:

$$P_{\text{apparent}} = 3,500 \text{ VA}$$

$$\cos \theta = 0.76 \text{ lagging}$$

$$I_{\text{effective}} = 18.0 \text{ A}$$

Solution:

$$\theta = \cos^{-1} 0.76$$

$$\theta = 40.53^\circ$$

$$S = 3500 \angle 40.53^\circ$$

$$S = 2660.23 + j2274.46; P = 2660.23 \text{ W}; Q_L = 2274.46 \text{ VAR}$$

$$P = I^2 R$$

$$R = 2660.23 / (18)^2$$

$$R = 8.21 \Omega$$

$$Q_L = I^2 X_L$$

$$X_L = 2274.46 / (18)^2$$

$$X_L = 7.018 \Omega$$

$$z = R + j X_L$$

$$z = 8.21 + j 7.018$$

$$z = 10.8 \angle 40.52^\circ \Omega$$

16) A two branch parallel circuit has a branch impedances of  $z_1 = 2.0 - j5.0 \Omega$ ,  $z_2 = 1 + j1 \Omega$ . Obtain the complete power triangle for the circuit if the two ohms resistor consumes 20 W.

Given:

$$z_1 = 2.0 - j5.0 \Omega$$

$$z_2 = 1 + j1 \Omega$$

$$P_{2\Omega} = 20 \text{ Watts}$$

Solution:

$$z_1 = 2 - j5 = 5.385 \angle -68.2^\circ$$

$$R_1 = 2\Omega$$

$$X_C = 5\Omega$$

$$z_2 = 1 + j1 \Omega = 1.414 \angle 45^\circ$$

$$I = \sqrt{20/2}$$

$$I = 3.16 \text{ A}$$

$$E = E_{z_1} = E_{z_2} = 3.16 (5.385)$$

$$E = 17.017 \text{ V}$$

$$I_2 = 17.017 \text{ V} / z_2$$

$$I_2 = (17.017) / (1.414)$$

$$I_2 = 12.03 \text{ A}$$

$$\begin{aligned} \text{Total Power} &= P_{2\Omega} + P_{1\Omega} \\ &= 20 + I_2^2(1) \\ &= 20 + (12.03)^2(1) \\ &= 164.7 \text{ W} \end{aligned}$$

$$Q_C = I_1^2(5) = (3.16)^2(5) = 49.928 \text{ VAR}$$

$$Q_L = I_2^2(1) = (12.03)^2(1) = 144.72 \text{ VAR}$$

$$Q_{NET} = Q_L - Q_C = 144.72 - 49.928 = 94.79 \text{ VAR (Inductive)}$$

$$\text{P.F.} = P / \sqrt{P^2 + Q_{NET}^2}$$

$$\text{P.F.} = P / \sqrt{(164.7)^2 + (95)^2}$$

$$\text{P.F.} = 0.866 \text{ Leading}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

17) A two branch parallel circuit with impedances  $z_1= 4 \angle -30^\circ$  and  $z_2 = 5 \angle 60^\circ \Omega$  has an effective voltage of 20V. Obtain the power triangles for the branches and combine them to obtain the power triangle.

Given:

$$Z_1= 4 \angle -30^\circ \Omega$$

$$Z_2 = 5 \angle 60^\circ \Omega$$

$$E= 20 \text{ V} = E_{z1}=E_{z2}$$

Solution:

$$I_1= E_{z1} / Z_1$$

$$I_1= 20/4$$

$$I_1= 5\text{A}$$

$$I_2= E_{z2} / Z_2$$

$$I_2=20 / 5$$

$$I_2= 4 \text{ A}$$

$$Z_1= 4 \angle -30^\circ = 3.46 -j2$$

$$P_1= I_1^2(3.46)$$

$$P_1=(5)^2(3.46)$$

$$P_1=86.5 \text{ W}$$

$$Z_2 = 5 \angle 60^\circ = 2.5 + j4.33$$

$$P_2= I_2^2(2.5)$$

$$P_2=(2.5)^2(2.5)$$

$$P_2= 40\text{W}$$

$$\text{Total Power} = P_1 + P_2$$

$$= 86.5 + 40$$

$$= 126.5 \text{ W}$$

$$Q_c= I_1^2(2)$$

$$Q_c= (5)^2(2)$$

$$Q_c= 50 \text{ VARS}$$

$$Q_L= I_2^2(4.33)$$

$$Q_L= (4)^2(4.33)$$

$$Q_L= 69.28 \text{ VARS}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

$$Q_{NET} = Q_L - Q_C$$

$$Q_{NET} = 69.28 - 50$$

$$Q_{NET} = 15.28 \text{ VARS Inductive}$$

Total Power Triangle:

$$S^2 = P_T^2 + Q_{net}^2$$

$$S = \sqrt{(126.5)^2 + (19.28)^2}$$

$$S = 127.9 \text{ VA}$$

$$\cos \theta = \text{P.F.} = P_T / S$$

$$\text{P.f.} = 126.5 / 127.9$$

$$\text{P.f.} = 0.988$$

$$S = 127.9 \angle 0.988^\circ$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

18) Obtain the complex power for the complete circuit below if branch 1 takes 8 kVAR.

Given:

$$Q_L = 8 \text{ kVAR}$$

$$X_{L1} = j5\Omega$$

$$R_2 = 4\Omega$$

$$X_{L2} = j2\Omega$$

Solution:

$$Q_L = 8000 \text{ VAR (inductive)}$$

$$Q_L = I_1^2 X_L$$

$$I_1^2 = 8000 / j5$$

$$I_1 = 40 \text{ A}$$

$$E = I_1 X_L$$

$$E = (40)(5)$$

$$E = 200 \text{ Volts}$$

$$Z_2 = 4 + j2\Omega$$

$$Z_2 = 4.47 \angle 26.56^\circ \Omega$$

$$I_2 = 200 / 4.47$$

$$I_2 = 44.47 \text{ A}$$

$$P_1 = I_2^2 (4)$$

$$P_1 = (44.47)^2 (4)$$

$$P_1 = 8,006.0 \text{ W}$$

$$Q_L = I_2^2 X_L$$

$$Q_L = (44.74)^2 (2)$$

$$Q_L = 4,003.3 \text{ VAR}$$

$$\text{Total Power} = 8,006.6 \text{ W}$$

$$Q_{\text{NET}} = P_T + Q_L$$

$$Q_{\text{NET}} = 8,000 + 4,003.3$$

$$Q_{\text{NET}} = 12,003.3 \text{ VAR}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

$$S^2 = P_T^2 + Q_{net}^2$$
$$S = \sqrt{(8,006.6)^2 + (12,003.3)^2}$$

$$S = 14,428.6 \text{ VA}$$

$$\cos \theta = \text{P.F.} = P_T / S$$

$$\text{P.f.} = 8,006.6 / 14,428.6$$

$$\text{P.f.} = 0.555 \text{ Lagging}$$

$$S = 14,428.6 \angle 56.28^\circ$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

19) A two element series circuit has average power of 940W and a power factor of 0.707 leading. Determine the circuit elements if the applied voltage  $V = 99.0 \cos(6000t + 30^\circ)$  V.

Given:

$$P_{ave} = 940 \text{ W} ; \text{ p.f} = 0.707$$

Solution:

$$E_{Effective} = 99.0 / \sqrt{2} = 70.0$$

$$P = V_{eff} \times I_{eff} \cos \theta$$

$$I_{eff} = 940 / [(70)(0.707)]$$

$$I_{eff} = 19.0 \text{ A}$$

$$I_{eff}^2 R = 940$$

$$R = 940 / 19^2$$

$$R = 2.6 \Omega$$

For leading power factor ,

$$\theta = \cos^{-1}(0.707)$$

$$\theta = -45^\circ$$

$$z = R - jX_C ; X_C = 2.6 \tan 45^\circ$$

Therefore,

$$2.60 = 1 / \omega C$$

$$C = 1 / [(2.60)(2\pi)(60)]$$

$$C = 64.1 \mu \text{ F}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

20) A two branch parallel circuit has a corresponding phasor diagram as shown below. Find the branch impedances  $Z_1$  and  $Z_2$ .

Solution using  $V_1$  as reference phasor

$$I_1 = 4.95 \angle -82.87^\circ \text{ A} ; I_2 = 6.67 \angle 90^\circ \text{ A}$$

$$Z_1 = V/I_1$$

$$Z_1 = (100 \angle 0^\circ) / (4.95 \angle -82.87^\circ)$$

$$Z_1 = 20.2 \angle 82.87^\circ$$

$$Z_1 = 2.5 + j20 \Omega$$

$$R_1 = 2.5 \Omega$$

$$X_{L1} = 20 \Omega$$

$$Z_2 = V/I_2$$

$$Z_2 = (100 \angle 0^\circ) / (6.67 \angle 90^\circ)$$

$$Z_2 = 15 \angle -90^\circ \Omega$$

$$Z_2 = 0 - j15 \Omega$$

$$R_2 = 0 \Omega$$

$$X_{C2} = 15 \Omega$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

21) A two branch parallel circuit has an applied voltage and resulting currents as given in the phasordigram shown in the figure. Find the branch impedances  $Z_1$  and  $Z_2$ .

Given:

$$I_1 = 6.5A$$

$$I_2 = 5A$$

$$V = 150V$$

Solution:

Using X as reference phasor

$$V_1 = 150 \angle -30^\circ$$

$$I_1 = 6.5 \angle 30^\circ$$

$$I_2 = 5 \angle -53.1^\circ$$

$$Z_1 = V / I_1$$

$$Z_1 = (150 \angle -30^\circ) / (6.5 \angle 30^\circ)$$

$$Z_1 = 23.07 \angle -60^\circ$$

$$Z_1 = 11.53 - j20\Omega$$

$$Z_2 = V / I_2$$

$$Z_2 = (150 \angle -30^\circ) / (5 \angle -53.1^\circ)$$

$$Z_2 = 30 \angle 23.1^\circ$$

$$Z_2 = 27.6 + j11.77\Omega$$

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

22. Given  $I_1 = 2 \angle -30^\circ$  and  $I_T = 4.47 \angle 33.4^\circ$  A. Find  $Z_2$

Solution:

$$I_2 = I_T - I_1$$

$$I_2 = (4.47 \angle 33.4^\circ) - (2 \angle -30^\circ)$$

$$I_2 = 2 + j3.46$$

$$I_2 = 4 \angle 60^\circ$$

$$I_1 Z_1 = I_2 Z_2$$

$$Z_2 = (I_1 Z_1) / I_2$$

$$Z_2 = [(2 \angle -30^\circ)(10)] / (4 \angle 60^\circ)$$

$$Z_2 = 0 - j5 \Omega$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

23. Use admittances to obtain  $Y_{eq}$  and  $Z_{eq}$  for the four branch parallel circuit shown in figure below. Compute  $I_T$  from the equivalent circuit.

Given:

$$Z_1 = 0 + j5\Omega = 5 \angle 90^\circ$$

$$Z_2 = 5 + j8.66 = 10 \angle 60^\circ$$

$$Z_3 = 15 + j0 = 15 \angle 90^\circ$$

$$Z_4 = 0 - j10 = 10 \angle -90^\circ$$

$$Y_{eq} = (Z_1)^{-1} + (Z_2)^{-1} + (Z_3)^{-1} + (Z_4)^{-1}$$

$$Y_{eq} = (5 \angle 90^\circ)^{-1} + (10 \angle 60^\circ)^{-1} + (15 \angle 90^\circ)^{-1} + (10 \angle -90^\circ)^{-1}$$

$$Y_{eq} = 0.22 \angle -58^\circ$$

$$Z_{eq} = Y_{eq}^{-1}$$

$$Z_{eq} = (0.22 \angle -58^\circ)^{-1}$$

$$Z_{eq} = 4.545 \angle 58^\circ$$

$$I_T = V / Z_{eq}$$

$$I_T = (150 \angle 45^\circ) / (4.545 \angle 58^\circ)$$

$$I_T = 33 \angle -13^\circ$$

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

24) Find the equivalent admittances and impedance of the three branch parallel circuit shown below.

Given:

$$Z_1 = 10 + j5 = 11.18 \angle 26.56^\circ$$

$$Z_2 = 5\Omega = 5 \angle 0^\circ$$

$$Z_3 = 2 + j8 = 8.24 \angle 76^\circ$$

Solution:

$$Y_{eq} = (Z_1)^{-1} + (Z_2)^{-1} + (Z_3)^{-1}$$

$$Y_{eq} = (11.18 \angle 26.56^\circ)^{-1} + (5 \angle 0^\circ)^{-1} + (8.24 \angle 76^\circ)^{-1}$$

$$Y_{eq} = 0.346 \angle -27^\circ$$

$$Z_{eq} = Y_{eq}^{-1}$$

$$Z_{eq} = (0.346 \angle -27^\circ)^{-1}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

25) Given:  $V = 50 \angle 30^\circ$ ;  $I_T = 27.9 \angle 57.8^\circ$  A. Determine the value of  $Z_1$  in the given figure.

Solution:

$$Z_{ab} = (Z_2 \times Z_3) / (Z_2 + Z_3)$$

$$Z_{ab} = (2-j2) \times (10) / (2-j2) + (10)$$

$$Z_{ab} = 2.325 \angle -35.53^\circ \Omega$$

$$I'' = V / Z_{ab}$$

$$I'' = (100 \angle 90^\circ) / (2.325 \angle -35.53^\circ \Omega)$$

$$I'' = -25 + j35 \text{ A}$$

$$I' = I_T - I''$$

$$I' = (-10.86 + j49) - (-25 + j35)$$

$$I' = 20 \angle 44.2^\circ \text{ A}$$

$$Z = V / I'$$

$$Z = (100 \angle 90^\circ) / (20 \angle 44.2^\circ)$$

$$Z = 5 \angle 45.8^\circ \Omega$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

26) Referring to figure below, determine the constants R and  $X_L$  if the total effective current is 29.9A, the current in the pure resistor is 8A and the current in the parallel  $R_L$  is 22.3 A.

Given:

$$I_T = 29.9A$$

$$I_1 = 22.3A$$

$$I_2 = 8A$$

Solution:

$$Z_{ab} = (Z_2 \times Z_3) / (Z_2 + Z_3)$$

$$Z_{ab} = (3-j4) \times (5) / (3-j4) + (5)$$

$$Z_{ab} = 2.79 \angle -26.56^\circ \Omega$$

$$I'' = V / Z_{ab}$$

$$I'' = (50 \angle 30^\circ) / (2.79 \angle -26.56^\circ \Omega)$$

$$I'' = 17.92 \angle 56.56^\circ A$$

$$I' = I_T - I''$$

$$I' = (29.9 \angle 57.8^\circ) - (17.92 \angle 56.56^\circ)$$

$$I' = 9.98 \angle 60^\circ A$$

$$Z = V / I'$$

$$Z = (50 \angle 30^\circ) / (9.98 \angle 60^\circ)$$

$$Z = 5 \angle -30^\circ \Omega$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

27) If  $V = 100 \angle 90^\circ$  and  $I_T = 50.2 \angle 102.5^\circ$  in the figure below, determine the value of  $Z_1$ .

Given:

$$Z_2 = 2 - j2 \Omega$$

$$Z_3 = 10 \Omega$$

Solution:

For resistive circuit, the current is in phase with the voltage thus;

$$I_2 = 8 \angle 0^\circ$$

$$I_1 = 22.3 \text{ A}$$

$$\cos \phi = [8^2 + (22.3)^2 - (29.9)^2] / (2)(8)(22.3)$$

$$\phi = \cos^{-1}(-0.9325)$$

$$\phi = 158.82^\circ$$

$$I_1 = 22.3 \angle -21.18^\circ$$

$$Z_1 = V / I_1$$

$$Z_1 = [(8)(15 \angle 0^\circ)] / (22.3 \angle -21.18^\circ)$$

$$Z_1 = 5.38 \angle 21.18^\circ$$

$$Y_1 = Z_1^{-1}$$

$$Y_1 = (5.38 \angle 21.18^\circ)^{-1}$$

$$Y_1 = 0.1733 + j0.067$$

$$R = 1 / 0.1733$$

$$R = 5.8 \Omega$$

$$X_L = 1 / 0.067$$

$$X_L = 14.9 \Omega$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

28) A voltmeter placed across the 3 ohms resistor shown, if the voltmeter reads 45 volts. What is the ammeter reading?

Solution:

$$I_{3\Omega} = 4.5 / 3 = 15A$$

$$R_{bc} = (5 \times 2) / (5 + 2) = 1.43\Omega$$

$$Z_1 = R_{ab} + 10$$

$$Z_1 = 1.43 + 10$$

$$Z_1 = 11.43\Omega$$

$$Z_{eq} = (Z_1 Z_2) / (Z_1 + Z_2)$$

$$Z_{eq} = (1.43)(3 + j3) / (1.43) + (3 + j3)$$

$$Z_{eq} = 3.28 \angle -33.25^\circ$$

$$I_{ac} = (15)(3 + j3) / 11.43$$

$$I_{ac} = 3.92 + j3.92$$

Ammeter Reading

$$I_{am} = I_{3\Omega} + I_{ac}$$

$$I_{am} = 15 + (3.92 + j3.92)$$

$$I_{am} = 19.4 \angle 11.71^\circ$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

29. In the circuit of figure below, the effective voltage between points A & B is 25V. Find the corresponding effective values of V and  $I_T$  (Hint: assume any convenient  $V'$  and determine the corresponding  $V_{AB}$  ; Then  $(V/25) = (V'/V_{ab'})$ )

Given:

$$V_{ab} = 25V$$

$$Z_1 = 5 + j3\Omega = 5.83 \angle 30.96^\circ$$

$$Z_2 = 10 + j0 = 10 \angle 0^\circ$$

Solution:

$$\text{Let } V' = 120V$$

$$I_1 = (120) / (5.83 \angle 30.96^\circ)$$

$$I_1 = 20.58 \angle -30.96^\circ A$$

$$I_2 = (120 \angle 0^\circ) / 10$$

$$I_2 = 12 \angle 0^\circ A$$

$$V_{AB}' = -I_1(5) + I_2(6)$$

$$V_{AB}' = [-(20.58 \angle -30.96^\circ A)(5)] / [(12 \angle 0^\circ)(6)]$$

$$V_{AB}' = 55.36 \angle -107.05^\circ V$$

Then;

$$V = 25(120 / 55.36)$$

$$V = 54.2 V$$

$$Z_T = [(10)(5.38 \angle 30.96^\circ)] / (15 + j3)$$

$$Z_T = 3.81 \angle 19.65^\circ \Omega$$

$$I_T = V / Z_T$$

$$I_T = 54.2 / 3.81$$

$$I_T = 14.22 A$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

30. A single-phase AC voltage of 240V is applied to series circuit whose impedance is  $10 \angle 60^\circ \Omega$ . Find R,X,P,Q and the power factor.

Solution:

$$R = 10 \cos 60^\circ$$

$$R = 5.0 \Omega$$

$$X = 10 \sin 60^\circ$$

$$X = 8.66 \Omega$$

$$I = (240 \angle 0^\circ) / (10 \angle 60^\circ)$$

$$I = 24 \angle -60^\circ \text{ A}$$

$$P = (24)^2 (5)$$

$$P = 2880 \text{ W}$$

$$Q = (24)^2 (8.66)$$

$$Q = 4988 \text{ VAR}$$

$$\text{p.f} = \cos [\tan^{-1}(Q/P)]$$

$$\text{p.f} = \cos [\tan^{-1}(4988/2880)]$$

$$\text{p.f} = 0.5$$

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

31. If a capacitor is connected in parallel with the circuit of the previous problem and if this capacitor supplies 1250 VAR, find the P and Q supplied by the 240V source, and find the resultant power factor.

Given:

$$P = 2880W$$

$$Q = 4988 \text{ VAR}$$

Solution:

$$Q = 4988 - 1250$$

$$Q = 3738 \text{ VAR}$$

$$\text{Power factor} = \cos [\tan^{-1}(Q/P)]$$

$$\text{p.f} = \cos [\tan^{-1}(3738/2880)]$$

$$\text{p.f} = 0.61$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

32. Find the equivalent impedance and equivalent admittance for the two branch parallel circuit shown in fig. below. Compute the current from each equivalent circuit.

Given:

$$Z_L = 10 + j20\Omega = 22.36 \angle 63.43^\circ$$

$$Z_C = 15 - j15\Omega = 21.21 \angle -45^\circ$$

Solution:

$$Z_{eq} = (Z_L \times Z_C) / (Z_L + Z_C)$$

$$Z_{eq} = (22.36 \angle 63.43^\circ \times 21.21 \angle -45^\circ) / (22.36 \angle 63.43^\circ + 21.21 \angle -45^\circ)$$

$$Z_{eq} = (474.25 \angle 18.43^\circ) / (25.5 \angle 11.319^\circ)$$

$$Z_{eq} = 18.6 \angle 7.12^\circ$$

$$Y_{eq} = Z_{eq}^{-1}$$

$$Y_{eq} = (18.6 \angle 7.12^\circ)^{-1}$$

$$Y_{eq} = 0.0538 \angle -7.12^\circ$$

$$I_1 = V/Z_L$$

$$I_1 = 200 \angle 0^\circ / (22.36 \angle 63.43^\circ)$$

$$I_1 = 8.94 \angle -63.43^\circ$$

$$I_1 = 4 - j8 \text{ A}$$

$$I_2 = V/Z_C$$

$$I_2 = 200 \angle 0^\circ / (21.21 \angle -45^\circ)$$

$$I_2 = 9.43 \angle 45^\circ$$

$$I_2 = 6.66 + j6.66 \text{ A}$$

$$I_T = I_1 + I_2$$

$$I_T = (4 - j8) + (6.66 + j6.66)$$

$$I_T = 10.66 - j1.34$$

$$I_T = 10.74 \angle -7.16^\circ$$

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

33. Find  $I_T$  in the two branch parallel circuit shown in figure below. Find the equivalent impedance from the ratio  $V/I_T$  and compare this with  $Z_{eq} = Z_1 Z_2 / Z_1 + Z_2$

Given:

$$Z_1 = 4 - j4 = 5.65 \angle -45^\circ$$

$$Z_2 = 5 + j8.66 = 9.99 \angle 59.99^\circ$$

Solution:

$$I_1 = V/Z_1$$

$$I_1 = (100 \angle 30^\circ) / (5.65 \angle -45^\circ)$$

$$I_1 = 17.7 \angle 75^\circ$$

$$I_2 = V/Z_2$$

$$I_2 = (100 \angle 30^\circ) / (9.99 \angle 59.99^\circ)$$

$$I_2 = 10 \angle -30^\circ$$

$$I_T = I_1 + I_2$$

$$I_T = (17.7 \angle 75^\circ) + (10 \angle -30^\circ)$$

$$I_T = 13.24 + j12.09$$

$$I_T = 17.9 \angle 42.4^\circ$$

$$Z_{eq} = (Z_L \times Z_C) / (Z_L + Z_C)$$

$$Z_{eq} = [(5.65 \angle -45^\circ) \times (9.99 \angle 59.99^\circ)] / [(5.65 \angle -45^\circ) + (9.99 \angle 59.99^\circ)]$$

$$Z_{eq} = 5.57 \angle -12.4^\circ$$

$$I = V / Z_{eq}$$

$$I = (100 \angle 30^\circ) / (5.57 \angle -12.4^\circ)$$

$$I = 17.9 \angle 42.4^\circ \text{ A}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

34. A resistor and an inductor are connected in parallel to a 120 volt 60 cycles source. If the total current and power in the circuit are 17A and 1800 Watts , calculate the values of R and L.

Given:

$$I_T = 17A$$

$$P_T = 1800W$$

$$V_T = 120V = V_R$$

Solution:

$$P_T = V_T I_T \cos \theta$$

$$\theta = \cos^{-1} [(120 \times 17) / 1800]$$

$$\theta = 28.0725^\circ$$

$$\cos \theta = I_R / I_T$$

$$I_R = (17) \cos 28.0725^\circ$$

$$I_R = 15A$$

$$V_R = I_R R$$

$$120 = (15A)R$$

$$R = 8\Omega$$

$$\sin \theta = I_L / I_T$$

$$I_L = (17) \sin 28.0725^\circ$$


$$I_L = 8A$$

$$X_L = 2 \pi fL$$

$$X_L = 15\Omega$$

$$L = (2 \pi)^{-1} (60) / 15$$

$$L = 0.0398 H$$

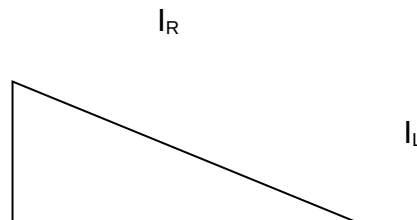

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

35. A single-phase inductive load draws 10 MW at 0.6 power factor lagging. Draw the power triangle and determine the reactive power of a capacitor to be connected in parallel with the load to raise the power factor to 0.85

Solution:

$$(10 / 0.6) \sin (\cos^{-1} 0.6) = 13.33$$

$$\cos^{-1} (0.85) = 31.79^\circ$$

$$10 \tan 31.79^\circ = 6.2 \text{ VAR}$$

$$Q_c = - (13.33 - 6.2)$$

$$Q_c = -7.13 \text{ Mvar}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

36. A resistor R are connected in parallel to an inductive resistance  $jX_L$  and the combination is connected in parallel to a 4 ohm resistor. The total current is 30A, the current through the parallel R and  $jX_L$  is 18 A while current through the 4 ohm resistor is 15A. Determine the unknown R and  $jX_L$ .

Solution:

$$\theta = 180 - \cos^{-1} [(I_1^2 + I_2^2 - I_T^2) / (2I_1 I_2)]$$

$$\theta = 180 - \cos^{-1} [(18^2 + 15^2 - 30^2) / (2)(18)(15)]$$

$$\theta = 49.4584^\circ$$

$$V_T = 4(15A)$$

$$V = 60V$$

$$I_R = I_1 \cos \theta$$

$$I_R = 18 \cos 49.4584^\circ$$

$$I_R = 11.7A$$

$$I_L = I_1 \sin \theta$$

$$I_L = 18 \sin 49.4584^\circ$$

$$I_L = 13.687A$$

$$R = V_T / I_R$$

$$R = 60V / 11.7A$$

$$R = 5.1282 \Omega$$

$$X_L = V_T / I_L$$

$$X_L = 60V / 13.687A$$

$$X_L = 4.3837 \Omega$$

Group IV	June
EE 3303	Engr.Kenneth F. Fajilan

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

37. A series combination of R and C is in parallel with a 20Ω resistor. A 60 Hz source resulting in a total current of 7.02A, a current through the 20Ω resistor is 6A and the current in the RC branch is 2.3A. Determine the R and C.

Solution:

$$\theta = \cos^{-1} [(I_T^2 - I_R^2 - I_Z^2) / (2I_R I_Z)]$$

$$\theta = \cos^{-1} [(7.02^2 - 6^2 - 2.3^2) / (2)(6)(2.3)]$$

$$\theta = 73.1715^\circ$$

$$V_T = (20\Omega)(6A)$$

$$V = 120V$$

$$Z = V_T / I_Z$$

$$Z = 120V / 2.3A$$

$$Z = 52.1739 \angle \theta \ \Omega$$

$$Z = 52.1739 \angle 73.1715^\circ \ \Omega$$

$$Z = 15.1048 + j 49.9396$$

Group IV	June
EE 3303	Engr.Kenneth F. Fajilan

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

38) A load of 300kW with a power factor of 0.65 lagging has the power factor improved to 0.90 lagging by the addition of parallel capacitors. What kVAR of capacitors does require to improved the power factor?

Given:

P= 300kW

Pf<sub>i</sub> = 0.65 lagging

Pf<sub>f</sub>= 0.90 lagging

Solution:

$$\theta_i = \cos^{-1} 0.65$$

$$\theta_i = 49.4584^\circ$$

$$\theta_f = \cos^{-1} 0.90$$

$$\theta_f = 25.8419^\circ$$

$$Q_{\text{req}} = P [\tan \theta_i - \tan \theta_f]$$

$$Q_{\text{req}} = 300\text{kW} (\tan 49.4584^\circ - \tan 25.8419^\circ)$$

$$Q_{\text{req}} = 205.4425\text{kVAR (leading)}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

39) A 20 ohm resistor is connected in series with a parallel combination of a capacitance C and 15mH pure inductance. At angular frequency  $\omega = 1000\text{rad/s}$ , find C such that the line current is  $45^\circ$  out of phase with the line voltage.

Given:

$$R = 20\Omega$$

$$L = 15\text{mH}$$

$$\omega = 1000\text{rad/s}$$

$$C = ?$$

Solution:

$$Z = R \pm jX$$

$$Z_T = 20 + [(j15)(-jX_C)] / (15 - X_C) j$$

$$Z_T = \infty$$

$$0 = 20 + [(j15)(-jX_C)] / (15 - X_C) j$$

$$X_C = 60\Omega$$

$$C = 1 / (2 \pi f X_C)$$

$$C = 1 / [(1000)(60)]$$

$$C = 16.6667 \mu\text{F}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

40) An inductive coil consumes 500W of power at 10A and 110V and 60Hz. Determine the resistance and the inductance of the coil.

Given:

$$P = 500W$$

$$I = 10A$$

Solution:

$$P_T = V_T I_T \cos \theta$$

$$\theta = \cos^{-1} [(110 \times 10) / 500]$$

$$\theta = 62.9643^\circ$$

$$Z_T = V_T / I_T$$

$$Z_T = 110 / 10$$

$$Z_T = 11\Omega$$

$$Z_T = 11 \angle 62.9643^\circ$$

$$Z_T = 5 + j.7980$$

$$X_L = 9.7980$$

$$X_L = 2 \pi fL$$

$$X_L = 9.7980$$

$$L = 9.7980 / (2 \pi)(60)$$

$$L = 25.9900H$$

$$R = 5\Omega$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

41) An inductive coil having a 30 ohm resistance and unknown reactance is connected in parallel with 100 ohm resistor. The combination is connected across a 100V 50/  $\pi$  Hz source. If the power delivered by the source is 400W, find the value of the inductance.

Solution;

$$P_T = P_1 + P_2$$

$$P_T = (I_1^2 R) + (V^2/R)$$

$$400 = (I_1^2 (30)) + (100^2/100)$$

$$I_1 = 3.1623 \text{ A}$$

$$Z = V_2 / I_2$$

$$Z = 100 / 3.1623$$

$$Z = 31.6266 \Omega$$

$$Z^2 = R^2 + X^2$$

$$(31.6266)^2 = 30^2 + X^2$$

$$X_L = 10$$

$$X_L = 2 \pi fL$$

$$L = 10 / (2 \pi (50 / \pi))$$

$$L = 0.1 \text{ H}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

42) A 250VA 0.5 lagging power factor load is connected in parallel to 180W 0.8 leading power factor load and the combination to 300VA 100 VAR inductive load. Determine the complex power for the combination of the three loads.

Given:

Load 1: 250VA, p.f 0.5 lagging

Load2: 180W, p.f 0.8 leading

Load 3: 300VA 100 VAR

Solution:

$$\theta_1 = \cos^{-1} 0.5$$

$$\theta_1 = 60^\circ$$

$$\theta_2 = \cos^{-1} 0.8$$

$$\theta_2 = 36.8699^\circ$$

$$S_2 = P_2 / \cos \theta_2$$

$$S_2 = 180 / \cos 36.8699^\circ$$

$$S_2 = 225 \text{ VA}$$

$$\theta_1 = \sin^{-1} Q/S$$

$$\theta_1 = \sin^{-1} 100/300$$

$$\theta_1 = 19.4712^\circ$$

$$S_T = S_1 + S_2 + S_3$$

$$S_T = (250 \angle 60^\circ) + (225 \angle -36.8699^\circ) + (300 \angle 19.4712^\circ)$$

$$S_T = 587.8427 + j 181.5062$$

$$S_T = 615.2265 \angle 17.1589^\circ$$

$$S_T = 615.2265 \text{ VA}$$

$$P = 587.8427 \text{ W}$$

$$Q = 181.5062 \text{ lagging}$$

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

43. A given load takes 40kVa at 0.5 lagging power factor while another load connected in parallel across the same source takes 80 kVa at 0.88 lagging power factor. Find the total reactive power.

Solution:

$$S_1 = 40 \text{ kVa @ } 0.5 \text{ lagging}$$

$$S_2 = 80 \text{ kVa @ } 0.88 \text{ lagging}$$

$$S_T = S_1 + S_2$$

$$S_T = 40 \angle \cos^{-1} 0.5 + 80 \angle \cos^{-1} 0.88$$

$$S_T = 40 \angle -60 + 80 \angle -28.357$$

$$S_T = 90400.42217 - j72638.12866^\circ \text{ kVa}$$

$$Q_T = 72638.9108 \text{ VAR}$$

44. An inductive reactance of  $10\Omega$  is connected in parallel with capacitive reactance of  $30\Omega$ . If the combination is connected in series with  $10\Omega$  resistance, solve for the total impedance of the circuit.

Solution:

$$z_T = \left[ \frac{1}{0+jX_L} + \frac{1}{0-jX_C} \right]^{-1} + 10$$

$$Z_T = \left[ -j\frac{1}{X_L} + j\frac{1}{X_C} \right]^{-1} + 10$$

$$Z_T = \left[ -j\frac{1}{10} + j\frac{1}{30} \right]^{-1} + 10$$

$$Z_T = j15 + 10$$

$$Z_T = 18.03 \angle 56.31^\circ$$

45. Two impedances  $Z_1 = 3+j4$ ,  $Z_2 = 5-j8.66 \Omega$  respectively are connected in parallel. If the combination is connected across a 240 V ac source, how much is the total power?

Solution:

$$Z_1 = 3+j4 = 5 \angle 53.13^\circ$$

$$Z_2 = 5-j8.66 = 9.99977 \angle -59.9993^\circ$$

$$I_1 = \frac{E}{Z_1}$$

$$I_1 = \frac{240 \angle 0}{5 \angle 53.13^\circ}$$

$$I_1 = 48 \angle -53.13^\circ$$

$$P_1 = I_1^2 R$$

$$P_1 = 48^2 \quad (3)$$

$$P_1 = 6912W$$

$$I_2 = \frac{E}{Z_2}$$

$$I_2 = \frac{240 \angle 0}{9.99977 \angle -59.9993^\circ}$$

$$I_2 = 24 \angle -59.9993^\circ$$

$$P_2 = I_2^2 R$$

$$P_2 = 24^2 \quad (5)$$

$$P_2 = 2880W$$

$$P_T = P_1 + P_2$$

$$P_T = 9792 W$$

46. A coil having a resistance of  $30\Omega$  and an inductance  $L$  is connected in parallel with a resistor having a resistance of  $100\Omega$ . The combination is connected across a  $100V$ ,  $60$  Hz source. If the power delivered by the source is  $400$  W, find the value of  $L$ .

Solution:

$$Y_T = \frac{1}{R_1 + jX_L} + \frac{1}{R_2}$$

$$Y_T = \frac{R_1 - jX_L}{R_1^2 + X_L^2} + \frac{1}{R_2}$$

$$Y_T = \left[ \frac{R_1}{R_1^2 + X_L^2} + \frac{1}{R_2} \right] - \frac{jX_L}{R_1^2 + X_L^2}$$

$$Y_T = G_T - j\beta_T$$

$$Y_T = \left[ \frac{30}{30^2 + X_L^2} + \frac{1}{100} \right] - j \frac{X_L}{30^2 + X_L^2}$$

$$P_T = E^2 G_T$$

$$400W = (100^2) \left( \frac{30}{30^2 + X_L^2} + \frac{1}{100} \right)$$

$$X_L = 10\Omega$$

$$X_L = 2\pi fL; L = \frac{X_L}{(2\pi f)}$$

$$L = \frac{10}{(2\pi)(60)}$$

$$L = 0.0265 \text{ H}$$

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

47. A parallel circuit consists of a resistor having a conductance of 4 mhos, an inductive reactor having a susceptance of 8 mhos and a capacitive reactor having a susceptance of 6 mhos. What is the impedance of the circuit?

Solutiuon:

$$G_T = 4\Omega$$

$$\beta_{TL} = 8\Omega$$

$$\beta_{TC} = 6\Omega$$

$$Y_T = 4 - j8 + j6$$

$$Y_T = 4 - j2$$

$$Z_T = \frac{1}{4 - j2}$$

$$Z_T = 0.2236 \angle 26.57^\circ$$

48. Two parallel branches have admittances of  $0.3+j0.4$  and  $0.2-j0.5$  respectively. If the current in the first branch is 11 A, determine the total current supplied to the combination.

Solution:

$$Y_T = Y_1 + Y_2$$

$$Y_T = 0.3 + j0.4 + 0.2 - j0.5$$

$$Y_T = 0.5 - j0.1$$

$$Z_1 = 2 \angle -53.13^\circ$$

$$E = IZ$$

$$E = (11)(2 \angle -53.13^\circ)$$

$$E = 22 \angle -53.13^\circ$$

$$Y_T = 0.5099 \angle -11.31^\circ$$

$$I_T = E X_T$$

$$22 \angle -53.13^\circ \quad || \quad 0.5099 \angle -11.31^\circ \angle i$$

$$I_T = 11.2178 \angle -64.44^\circ$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

49. Two impedances  $Z_1 = 3+j4$  and  $Z_2 = R+j0$  are connected in parallel. Determine R so that the power factor of the circuit is 0.9 lagging.

Solution:

$$Y_T = \frac{1}{3+j4} + \frac{1}{R_2}$$

$$Y_T = \frac{1}{R_1 + jX_L} + \frac{1}{R_2}$$

$$Y_T = \frac{R_1 - jX_L}{R_1^2 + X_L^2} + \frac{1}{R_2}$$

$$Y_T = \left[ \frac{R_1}{R_1^2 + X_L^2} + \frac{1}{R_2} \right] - j \frac{X_L}{R_1^2 + X_L^2}$$

$$Y_T = \left[ \frac{3}{3^2 + 4^2} + \frac{1}{R_2} \right] - j \frac{4}{3^2 + 4^2}$$

$$Y_T = G_T - j \beta_T$$

$$Y_T = 0.12 + \frac{1}{R_2} - j0.16$$

$$\tan 25.84^\circ = \frac{0.16}{0.12 + \frac{1}{R_2}}$$

$$R = 4.75 \Omega$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

50. An inductive coil with a resistance R and inductance L is connected in parallel with a  $30\ \Omega$  resistor. The combination is then connected across a 60 Hz source. If the currents in the coil, resistor and total are 6,4 and 8 A respectively. Determine the inductance of the coil.

Solution:

$$E = (30)(4)$$

$$E = 120\text{ V}$$

$$\beta = \cos^{-1} \left[ \frac{6^2 + 4^2 - 8^2}{(2)(6)(4)} \right]$$

$$\beta = 104.4775^\circ$$

$$\theta = 180 - \beta$$

$$\theta = 75.52^\circ$$

$$I = \frac{E}{Z}; Z = \frac{120}{6} = 20\ \Omega$$

$$Z = 20 \angle 75.52^\circ$$

$$Z = 5.0008 + j 19.36$$

$$R = 5.0008\ \Omega$$

$$X_L = 19.36\ \Omega$$

$$L = \frac{19.36}{(2\pi)(60)}$$

$$L = 0.0514\text{ H}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

51. Two circuits, the impedance of which are given by  $Z_1 = 10 + j15$  and  $Z_2 = 6 - j8$  ohms are connected in parallel. If the total current supplied is 15A, what is the power taken by each branch? Find also the p.f. of individual circuits and of combination. Draw the vector diagram.

Solution:

$$\text{Let } I = 15 \text{ cjs } 0^\circ \text{ A ; } Z_1 = 10 + j15 = 18 \text{ cjs } 57^\circ \Omega$$

$$Z_2 = 6 - j8 = 10 \text{ cjs } -53.1^\circ \Omega$$

Getting the total impedance:

$$Z_T = Z_1 Z_2 / (Z_1 + Z_2) = [ (10 + j15) (6 - j8) ] / (16 + j17)$$

$$Z_T = 9.67 - j3.6 \Omega = 10.3 \text{ cjs } -20.4^\circ \Omega$$

Applied voltage is given by:

$$V = I Z_T = (15 \text{ cjs } 0^\circ) (10.3 \text{ cjs } -20.4^\circ) = 154.5 \text{ cjs } -20.4^\circ \text{ V}$$

$$I_1 = V / Z_1 = (154.5 \text{ cjs } -20.4^\circ) / (18 \text{ cjs } 57^\circ) = 8.58 \text{ cjs } -77.4^\circ \text{ A}$$

$$I_2 = V / Z_2 = (154.5 \text{ cjs } -20.4^\circ) / (10 \text{ cjs } -53.1^\circ) = 15.45 \text{ cjs } 32.7^\circ \text{ A}$$

We could also find branch currents as under:

$$I_1 = (I Z_2) / (Z_1 + Z_2) \text{ and } I_2 = (I Z_1) / (Z_1 + Z_2)$$

It is seen from the phasor diagram that  $I_1$  lags behind  $V$  by  $(77.4^\circ - 20.4^\circ) = 57^\circ$  and  $I_2$  leads it by  $(32.7^\circ + 20.4^\circ) = 53.1^\circ$

Therefore:

$$P_1 = I_1^2 R_1 = (8.58)^2 \times 10 = 736 \text{ W; p.f.} = \cos 57^\circ = 0.544 \text{ (lag)}$$

$$P_2 = I_2^2 R_2 = (15.45)^2 \times 6 = 1432 \text{ W; p.f.} = \cos 53.1^\circ = 0.6$$

Combined p.f.:

$$\text{p.f.} = \cos 20.4^\circ = 0.937 \text{ (lead)}$$

52. Two impedance  $Z_1 = 8 + j6 \Omega$  and  $Z_2 = 3 - j4 \Omega$  are in parallel. If the total current of the combination is 25 A, find the current taken and power consumed by each impedance.

Solution:

$$Z_1 = (8 + j6) = 10 \text{ cjs } 36.87^\circ \Omega$$

$$Z_2 = (3 - j4) = 5 \text{ cjs } -53.1^\circ \Omega$$

$$Z_T = Z_1 Z_2 / (Z_1 + Z_2) = [(8 + j6)(3 - j4)] / (11 + j2)$$

$$Z_T = (50 \text{ cjs } -16.23^\circ) / (11.18 \text{ cjs } 10.3^\circ) = 4.47 \text{ cjs } -26.53^\circ \Omega$$

Let:  $I_T = 25 \text{ A}$

$$V = I_T Z_T = (25 \text{ cjs } 0^\circ) (4.47 \text{ cjs } -26.53^\circ) = 111.75 \text{ cjs } -26.53^\circ \text{ V}$$

$$I_1 = V / Z_1 = (111.75 \text{ cjs } -26.53^\circ) / (10 \text{ cjs } 36.87^\circ) = 11.175 \text{ cjs } -63.4^\circ \text{ A}$$

$$I_2 = V / Z_2 = (111.75 \text{ cjs } -26.53^\circ) / (5 \text{ cjs } -53.1^\circ) = 22.35 \text{ cjs } 26.57^\circ \text{ A}$$

The phase difference between  $V$  and  $I_1$  is  $(63.4^\circ - 26.53^\circ) = 36.87^\circ$  with the current lagging. Hence,  $\cos \theta_1 = \cos 36.87^\circ = 0.8$ .

$$\text{Power consumed in } Z_1 = VI_1 \cos \theta_1 = [(11.175)(111.75)(0.8)] = 990 \text{ W}$$

$$\text{Similarly, } \theta_2 = 26.57^\circ - (-26.53^\circ) = 53.1^\circ$$

$$\cos \theta_2 = \cos 53.1^\circ = 0.6$$

$$\text{Power consumed in } Z_2 = VI_2 \cos \theta_2 = [(111.75)(22.35)(0.6)] = 1499 \text{ W}$$

53. A mercury vapour lamp unit consist of a 25  $\mu\text{F}$  condenser in parallel with a series circuit containing the resistive lamp and a reactor of negligible resistance. The whole unit takes 400 W at 240 V, 50 Hz at unity p.f.. What is the voltage across the lamp?

Solution:

$$X_C = [ 1 / (2\pi fC) ] = [ 1 / (2\pi) (50) (25 \times 10^{-6}) ] = 127.3 \Omega$$

$$I_C = V / X_C = ( 240 / 127.3 ) = 1.885 \text{ A}$$

$$W = VI \cos \phi = VI$$

$$I = ( W / V ) = ( 400 / 240 ) = 1.667 \text{ A}$$

Since the vector sum of  $I_C$  and  $I_1$  gives the total current  $I$ , it is understood that  $\tan \phi_1 = I_C / I = 1.885 / 1.667 = 1.13077$ . Hence,  $\phi_1 = 48.5^\circ$  lag. The applied voltage  $V$  is the vector sum of the drop across the resistive lamp which is in phase with  $I_1$  and drop across the coil which leads  $I_1$  by  $90^\circ$ .

Voltage across the lamp:

$$V = V \cos \phi_1 = 240 \times \cos 48.5^\circ = 240 \times 0.662 = 159 \text{ V}$$

54. The currents in each branch of a two-branched parallel circuit are given by the expression  $i_a = 7.07 \sin(314t - \pi/4)$  and  $i_b = 21.2 \sin(314t + \pi/3)$ . The supply voltage is given by the expression  $v = 354 \sin 314t$ . derive a similar expression for the supply current and calculate the ohmic value of the component, assuming two pure components in each branch. State whether the reactive components are inductive or capacitive.

Solution:

By inspection, we find that  $i_a$  lags the voltage by  $\pi/4$  radian or  $45^\circ$  and  $i_b$  leads it by  $\pi/3$  radian or  $60^\circ$ . Hence, branch A consists of a resistance in series with a pure inductive reactance. Branch B consists of a resistance in series with pure capacitive reactance.

Maximum value of current in branch A is 7.07 A and in branch B is 21.2 A. the resultant current can be found vectorially.

$$X_{\text{comp}} = (21.2 \cos 60^\circ) + (7.07 \cos 45^\circ) = 15.6 \text{ A}$$

$$Y_{\text{comp}} = (21.2 \sin 60^\circ) - (7.07 \sin 45^\circ) = 13.36 \text{ A}$$

Maximum value of the resultant current is:

$$I_R^2 = (15.6)^2 + (13.36)^2$$

$$I_R = 20.55 \text{ A}$$

$$\theta = \tan^{-1} (13.36 / 15.6) = \tan^{-1} (0.856) = 40.5^\circ \text{ (leading)}$$

Hence, the expression for the supply current is  $i = 20.55 \sin(314t + 40.5^\circ)$

$$Z_A = 354/7.07 = 50 \Omega ; \cos \theta_A = \cos 45^\circ = 0.7071$$

$$R_A = Z_A \cos \theta_A = (50) (0.7071) = 35.4 \Omega$$

$$X_L = Z_A \sin \theta_A = (50) (0.7071) = 35.4 \Omega$$

$$Z_B = 354/20.2 = 17.5 \Omega$$

$$R_B = 17.5 \times \cos 60^\circ = 8.75 \Omega$$

$$X_C = 17.5 \times \sin 60^\circ = 15.16 \Omega$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

55. A total current of 10 A flows through the parallel combination of three impedances:  $(2 - j5)\Omega$ ,  $(6 + j3)\Omega$ , and  $(3 + j4)\Omega$ . Calculate the current flowing through each branch. Find also the p.f. of the combination.

Solution:

Let  $Z_1 = (2 - j5)\Omega$ ,  $Z_2 = (6 + j3)\Omega$ , and  $Z_3 = (3 + j4)\Omega$

$$Z_1Z_2 = (2 - j5)(6 + j3) = 27 - j24 \Omega$$

$$Z_2Z_3 = (6 + j3)(3 + j4) = 6 + j33 \Omega$$

$$Z_3Z_1 = (3 + j4)(2 - j5) = 26 - j7 \Omega$$

$$Z_1Z_2 + Z_2Z_3 + Z_3Z_1 = (27 - j24) + (6 + j33) + (26 - j7) = 59 + j2 \Omega$$

Getting the currents:

$$I_1 = I \cdot \{(Z_2Z_3) / [(Z_1Z_2) + (Z_2Z_3) + (Z_3Z_1)]\} = [(10 + j0)(6 + j33) / (59 + j2)] = 1.21 + j5.55 \text{ A}$$

$$I_2 = I \cdot \{(Z_1Z_3) / [(Z_1Z_2) + (Z_2Z_3) + (Z_3Z_1)]\} = [(10 + j0)(26 - j7) / (59 + j2)] = 4.36 - j1.33 \text{ A}$$

$$I_3 = I \cdot \{(Z_2Z_1) / [(Z_1Z_2) + (Z_2Z_3) + (Z_3Z_1)]\} = [(10 + j0)(27 - j24) / (59 + j2)] = 4.43 - j4.22 \text{ A}$$

For the total impedance:

$$Z_T = \{(Z_1Z_2Z_3) / [(Z_1Z_2) + (Z_2Z_3) + (Z_3Z_1)]\} = [(2 - j5)(6 + j33) / (59 + j2)] = 3.01 + j0.51 \Omega$$

$$V = (10 \text{ cjs } 0^\circ)(3.05 \text{ cjs } 9.6^\circ) = 30.5 \text{ cjs } 9.6^\circ$$

Combination p.f.:

$$\text{p.f.} = \cos 9.6^\circ = 0.986 \text{ (lag)}$$

56. Two impedances  $Z_1 = (6 - j8)$  ohms and  $Z_2 = (16 + j12)$  ohms are connected in parallel. If the total current of the combination is  $(20 + j10)$  A. Find the complexor for power taken by each impedance.

Solution:

Finding out the applied voltage:

$$Y = Y_1 + Y_2 = [ 1 / (6 - j8) ] + [ 1 / ( 16 + j 12) ] = (0.06 + j0.08) + (0.04 + j0.03) = 0.10 + j0.11 = 0.1118 \text{ cjs } 26^\circ 34'$$

$$I = 20 + j10 = 22.36 \text{ cjs } 26^\circ 34' \text{ A}$$

$$V = I / Y = (22.36 \text{ cjs } 26^\circ 34') / (0.1118 \text{ cjs } 26^\circ 34')$$

57. The power factor for the circuit, overall, has been substantially improved. The main current has been decreased from 1.41 amps to 994.7 milliamps, while the power dissipated at the load resistor remains unchanged at 119.365 watts. The power factor is much closer to being 1:

Solution:

P.f. = true power / apparent power

P.f. = 119.365W / 119.366 VA

P.f. = 0.9999887

impedance (polar) angle = 0.272

$\cos 0.272 = 0.9999887$

Group IV	June
EE 3303	Engr.Kenneth F. Fajilan

58. Calculate the current in this circuit, and also the amount of mechanical power (in units of "horsepower") required to turn this alternator (assume 100% efficiency): given, volts and 3.4 resistance.

Solution:

$$I = V / R$$

$$I = 480 / 3.4$$

$$I = 141.18 \text{ A}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

59. A 50-microfarad is connected in series with a coil 50 ohms resistance and 150-mh inductance. The source voltage is  $100 \sin(\omega t - 30^\circ)$  V. What is the maximum power?

Solution:

$$X_L = \omega L = 377(0.150) = 56.55\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{377(50 \times 10^{-6})} = 53.05\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{50^2 + (56.55 - 53.05)^2}$$

$$Z = 50.122\Omega$$

$$\Theta_L = \cos^{-1} \frac{R}{Z} = \cos^{-1} \left( \frac{50}{50.122} \right) = 3.998^\circ$$

$$\Theta_L \approx 4^\circ$$

$$I_m = \frac{E_M}{Z} = \frac{100 \angle -30^\circ}{50.122 \angle 4^\circ} = 1.995 \angle -34^\circ$$

$$P_m = E_m I_m \cos \Theta = (100)(1.995) \cos 4^\circ$$

$$P_m = 199 \text{ W}$$

60.

A load of  $20 + j35$  is connected across a 220 volts source. Determine the power factor and the VARS.

Solution:

$$Z = 20 + j35 = 40.31 \angle 60.255^\circ$$
$$\text{pf} = \cos \Theta = \cos 60.255^\circ = 0.496$$

$$\text{pf} = 49.6 \%$$

$$Q = EI \sin \Theta = \frac{E^2}{Z} \sin \Theta = \frac{220^2}{40.31} \sin 60.255^\circ$$

$$Q = 1042.25 \text{ VARS}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

61. The network is part of the schematic describing an industrial electronic sensing device. What is the total impedance of the circuit at 2 kHz?

Solution:

$$Z_1 = 50 + 1/j\omega C = 50 + 1/(2\pi)(2 \times 10^3)(2 \times 10^{-6}) \\ = 50 - j39.79$$

$$Z_2 = 80 + j\omega L = j(2\pi)(2 \times 10^3)(2 \times 10^{-6}) \\ = 80 + j125.66$$

$$Z_3 = 100$$

$$1/Z = 1/Z_1 + 1/Z_2 + 1/Z_3$$

$$1/Z = 10^{-3} (10 - j12.24 + j9.745 + 3.605 - j5.663)$$

$$Z = (25.85 + j4.082) \times 10^{-3} \\ = 26.17 \times 10^{-3} \angle 8.97^\circ$$

$$Z = 38.21 \angle -8.97^\circ \Omega$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

62. Two electric units are connected across a source whose frequency is 50 cps. If the voltage drop across the units are 115 and 90 volts and they are out of phase by  $90^\circ$ , what is the equation of the voltage across the source?

Solution:

$$E_T = \sqrt{E_1^2 + E_2^2}$$

$$= \sqrt{115^2 + 90^2}$$

$$E_T = 5 \sqrt{853} = 146.031$$

$$\Theta = \tan^{-1} \left( \frac{90}{115} \right)$$

$$\Theta = 38.0470^\circ$$

$$E_{Mt} = E_T \sqrt{2}$$

$$= 146.031 ( \sqrt{2} )$$

$$E_{Mt} = 206.5188 \text{ V}$$

$$\omega = 2\pi f$$

$$= 2\pi (50)$$

$$\omega = 314$$

$$E_t = 206.52 \sin (314t + 38.05^\circ) \text{ V}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

63. An impedance draws a current of 24 A at 0.8 lagging power factor from a source voltage of 240V, 60 Hz. What is the current when resistance is reduced by 50%?

Solution:

$$Z = \frac{e}{i} = \frac{240}{24} = 10\Omega$$

$$\text{Pf} = \frac{R}{Z}$$

$$R = Z (\text{Pf}) = (10) (0.8) = 8\Omega$$

$$\begin{aligned} X_L &= \sqrt{Z^2 - R^2} \\ &= \sqrt{10^2 - 8^2} \end{aligned}$$

$$X_L = 6\Omega$$

When  $R = 4\Omega$

$$\begin{aligned} Z &= \sqrt{R^2 + X_L^2} \\ &= \sqrt{4^2 + 6^2} \end{aligned}$$

$$Z = 2\sqrt{13} \Omega$$

$$I = \frac{e}{z} = Z = \frac{240 \text{ V}}{2\sqrt{13}\Omega}$$

$$I = 33.2820 \text{ A}$$

64. A single phase load takes 60 kW at 80% pf lagging from a 220 V, 50 Hz supply. If the supply is made 60 Hz, with the voltage remaining the same, what will be the kW load at 60 Hz?

Solution:

At 50 Hz:

$$Z = \frac{E^2 \cos \theta}{P} = \frac{(220)^2 (0.8)}{60000} = 0.645 \text{ ohms}$$

$$\theta = \cos^{-1} 0.8 = 36.869^\circ$$

$$R = Z \cos \theta = 0.645(0.8) = 0.516 \text{ ohms}$$

$$X_L = Z \sin \theta = 0.645(\sin 36.869^\circ) = 0.387 \text{ ohms}$$

$$L = \frac{X_L}{2\pi f} = \frac{0.387}{2\pi(50)} = 1.232 \text{ mH}$$

At 60 Hz:

$$X_L = 2\pi fL = 2\pi(60)(1.232 \times 10^{-3}) = 0.464 \text{ ohms}$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{(0.516)^2 + (0.464)^2} = 0.694 \text{ ohms}$$

$$\cos \theta = \frac{R}{Z} = \frac{0.516}{0.694} = 0.744$$

$$P = \frac{E^2 \cos \theta}{Z} = \frac{(220)^2 (0.744)}{0.694} = 51,887.03 \text{ W}$$

65. An inductive coil takes a current of 2 A and consumes 200 W when connected to a 220 v AC supply. A second coil when connected across the same supply takes 3 A and 300 W. Find the total power when the two coil are connected in series to this supply.

Solution:

$$R_a = \frac{P_a}{I_a^2} = \frac{200}{2^2} = 50 \text{ ohms}$$

$$Z_a = \frac{E}{I_a} = \frac{220}{2} = 110 \text{ ohms}$$

$$X_a = \sqrt{Z_a^2 - R_a^2} = \sqrt{110^2 - 50^2} = 97.980 \text{ ohms}$$

$$R_b = \frac{P_b}{I_b^2} = \frac{300}{3^2} = 33.333 \text{ ohms}$$

$$Z_b = \frac{E}{I_b} = \frac{220}{3} = 73.333 \text{ ohms}$$

$$X_b = \sqrt{Z_b^2 - R_b^2} = \sqrt{73.333^2 - 33.333^2} = 65.320 \text{ ohms}$$

$$Z_t = \sqrt{(R_a + R_b)^2 + (X_a + X_b)^2}$$

$$Z_t = \sqrt{(50 + 33.333)^2 + (97.980 + 65.320)^2}$$

$$Z_t = 183.333 \text{ ohms}$$

$$I_t = \frac{E}{Z_t} = \frac{220}{183.333} = 1.20 \text{ A}$$

$$P_t = I_t^2 R_t = (1.20)^2 (50 + 33.333)$$

$$P_T = 120 \text{ W}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

66. A current of 10 A and a power factor of 0.8 lagging is taken from a single phase 250 volt supply. The reactive power of the system is?

Solution:

$$\theta = \cos^{-1} 0.8 = 36.869^\circ$$

$$Q = EI \sin \theta$$

$$Q = (250)(10) \sin 36.869^\circ$$

$$Q = 1500 \text{ VARS}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

67. A coil of 50-ohm resistance and of 150 mH inductance is connected in parallel with a 50  $\mu$ F capacitor. What is the power factor of the circuit?

Solution:

$$X_L = \omega L = (377) (0.15) = 56.55 \Omega$$

$$X_C = 1 / \omega C = 1 / (377) (50 \times 10^{-6}) = 53.05 \Omega$$

$$(1 / Z_T) = (1 / Z_1) + (1 / Z_2) = [1 / (50 + j56.55)] + (1 / -j53.05)$$

$$(1 / Z_T) = [1 / (0.0125 \text{ cjs } 45.744^\circ)]$$

$$Z_T = 80 \text{ cjs } -45.744^\circ \Omega$$

$$\text{Pf} = \cos -45.744^\circ$$

$$\text{Pf} = 0.7$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

68. The impedance  $Z_1 = (6 + j8) \Omega$ ,  $Z_2 = (8 - j6) \Omega$ ,  $Z_3 = (10 + j0) \Omega$  measured at 50 Hz, form three branches of a parallel circuit. This circuit is fed from a 100 V, 50 Hz supply. A purely reactive (inductive or capacitive) circuit is added as the fourth parallel branch to the above three-branched parallel circuit so as to draw minimum current from the source. Determine the value of L or C to be used in the fourth branch and also find the minimum current.

Solution:

Total admittance of the three-branched parallel circuit:

$$Y = [ 1 / (6 + j8) ] + [ 1 / (8 - j6) ] + [ 1 / (10 + j0) ] = 0.06 - j0.08 + 0.08 + j0.06 + 0.1 = 0.24 - j0.02 \text{ Siemens}$$

Current taken would be minimum when net susceptance is zero. Since combined susceptance is inductive, it means that we must add capacitive susceptance to neutralize it. Hence, we must connect a pure capacitor in parallel with the above circuit such that its susceptance equals  $+j0.02 \text{ S}$ .

$$1 / X_C = 0.02 \text{ or } 2\pi / C = 0.02; C = 0.2/314 = 63.7 \mu\text{F}$$

$$\text{Admittance of four parallel branches} = (0.24 - j0.02) + j0.02 = 0.24 \text{ S}$$

$$\text{Minimum current drawn by the circuit} = 100 \times 0.24 = 24 \text{ A}$$

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

69.

A current of 8 A and a power factor of 0.8 lagging is taken from a single phase 220 volt supply. The reactive power of the system is?

Solution:

$$\theta = \cos^{-1} 0.8 = 36.869^\circ$$

$$Q = E I \sin \theta$$

$$Q = (220)(8) \sin 36.869^\circ$$

$$Q = 1055.98 \text{ VARS}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

70. A single phase load takes 55 kW at 70% pf lagging from a 240 V, 50 Hz supply. If the supply is made 60 Hz, with the voltage remaining the same, what will be the kW load at 60 Hz?

Solution:

At 50 Hz:

$$Z = \frac{E^2 \cos \theta}{P} = \frac{(240)^2 (0.7)}{55000} = 0.733 \text{ ohms}$$

$$\theta = \cos^{-1} 0.7 = 45.57^\circ$$

$$R = Z \cos \theta = 0.733(0.7) = 0.513 \text{ ohms}$$

$$X_L = Z \sin \theta = 0.733(\sin 45.57^\circ) = 0.523$$

$$L = \frac{X_L}{2\pi f} = \frac{0.523}{2\pi(50)} = 1.66 \text{ mH}$$

At 60 Hz:

$$X_L = 2\pi fL = 2\pi(60)(1.666 \times 10^{-3}) = 0.628 \text{ ohms}$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{(0.513)^2 + (0.628)^2} = 0.81 \text{ ohms}$$

$$\cos \theta = \frac{R}{Z} = \frac{0.513}{0.81} = 0.633$$

$$P = \frac{E^2 \cos \theta}{Z} = \frac{(240)^2 (0.633)}{0.81} = 45013.33 \text{ W}$$

$$P = 45 \text{ kW}$$

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

71. A coil of 40-ohm resistance and of 150 mH inductance is connected in parallel with a 50  $\mu$ F capacitor. What is the power factor of the circuit?

Solution:

$$X_L = \omega L = (377) (0.15) = 56.55 \Omega$$

$$X_C = 1 / \omega C = 1 / (377) (40 \times 10^{-6}) = 66.31 \Omega$$

$$(1 / Z_T) = (1 / Z_1) + (1 / Z_2) = [1 / (40 + j56.55)] + (1 / -j66.31)$$

$$(1 / Z_T) = [1 / (0.0037 \text{ cjs } 145.74^\circ)]$$

$$Z_T = 277.78 \text{ cjs } -145.74 \Omega$$

$$\text{Pf} = \cos -145.74^\circ$$

$$\text{Pf} = 0.82$$

72. Find the equivalent admittances and impedance of the three branch parallel circuit shown below.

Given:

$$Z_1 = 10 + j2 = 10.19 \angle 11.31^\circ$$

$$Z_2 = 2\Omega = 2 \angle 0^\circ$$

$$Z_3 = 5 + j8 = 9.43 \angle 57.99^\circ$$

Solution:

$$Y_{eq} = (Z_1)^{-1} + (Z_2)^{-1} + (Z_3)^{-1}$$

$$Y_{eq} = (10.19 \angle 11.31^\circ)^{-1} + (2 \angle 0^\circ)^{-1} + (9.43 \angle 57.99^\circ)^{-1}$$

$$Y_{eq} = .0052 \angle -69.12^\circ$$

$$Z_{eq} = Y_{eq}^{-1}$$

$$Z_{eq} = (192.18 \angle 69.12^\circ)^{-1}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

73. Given:  $Z_1 = -j2.5 \text{ ohms}$ ;  $Z_2 = j4 \text{ ohms}$ ;  $Z_3 = 5 \text{ ohms}$ ;  $Z_4 = 1 + j5 \text{ ohms}$ . If the four impedances are connected in parallel, find the equivalent impedance in ohms.

Solution:

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \frac{1}{Z_4}$$

$$\frac{1}{Z_t} = \frac{1}{-j2.5} + \frac{1}{j4} + \frac{1}{5} + \frac{1}{1+j5}$$

$$\hookrightarrow j0.4 - j0.25 + 0.2 + \frac{1}{5.1 \angle 78.69^\circ}$$

$$\hookrightarrow 0.2 + j0.15 + 0.196 \angle -78.69^\circ$$

$$\hookrightarrow 0.2 + j0.15 + 0.0384 - j0.1922$$

$$\frac{1}{Z_t} = 0.2384 - j0.0422 = 0.2421 \angle -10.038^\circ$$

$$Z_t = \frac{1}{0.2421 \angle -10.038^\circ} = 4.13 \angle 10.038^\circ = 4.066 + j0.719 \Omega$$

$$Z_t \cong 4.1 + j0.72 \Omega$$

74. Three impedances  $Z_a = 3 + j4$  ohms,  $Z_c = 4 - j4$  ohms and  $Z_r = 0 + j3$  ohms are connected in parallel. Solve for the power factor of the combination.

Solution:

$$\frac{1}{Z_t} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} = \frac{1}{3+j4} + \frac{1}{4-j4} + \frac{1}{j3}$$

$$\frac{1}{5 \angle 53.13^\circ} + \frac{1}{5.656 \angle -45^\circ} - j0.333$$

$$\hookrightarrow 0.2 \angle -53.13^\circ + 0.1768 \angle 45^\circ - j0.333$$

$$\hookrightarrow 0.12 - j0.16 + 0.125 - j0.125 - j0.333$$

$$\hookrightarrow 0.245 - j0.368 = 0.442 \angle -56.34^\circ$$

$$Z_t = \frac{1}{0.442 \angle -56.34^\circ} = 2.262 \angle 56.34^\circ$$

$$pf = \cos 56.34^\circ$$

$$pf = 0.554 \text{ lagging}$$

75. A coil of a 50-ohm resistance and of 150 mH inductance is connected in parallel with a 50  $\mu$  F capacitor. What is the power factor of the circuit?

Solution:

$$X_L = \omega L = 377(0.15) = 56.55 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{377(50 \times 10^{-6})} = 53.05 \Omega$$

$$\frac{1}{Z_t} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{50 + j56.55} + \frac{1}{-j53.05}$$

$$\angle \frac{1}{75.484 \angle 48.517^\circ} = j0.01885$$

$$\angle 0.0132 \angle -48.517^\circ + j0.01885$$

$$\angle 0.00874 - j0.00988 + j0.01885$$

$$\angle 0.00874 + j0.00897 = 0.0125 \angle 45.744^\circ$$

$$Z_t = \frac{1}{0.0125 \angle 45.744^\circ}$$

$$\angle 80 \angle -45.744^\circ$$

$$pf = \cos(-45.744^\circ)$$

$$pf \cong 0.7$$

Group IV

June

EE 3303

Engr. Kenneth F. Fajilan

76. A resistor of 50 ohms and an impedance of  $100 + j50$  ohms are connected in parallel across a 220 volts supply. What is the power factor of the load?

Solution:

$$\frac{1}{Z_t} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{50} + \frac{1}{100 + j50}$$

$$\hookrightarrow 0.02 + \frac{1}{111.803 \angle 26.565^\circ}$$

$$\hookrightarrow 0.02 + 0.00894 \angle -26.565^\circ$$

$$\hookrightarrow 0.02 + 0.008 - j0.004$$

$$\hookrightarrow 0.028 \angle -j0.004$$

$$\hookrightarrow 0.0283 \angle 8.13^\circ$$

$$Z_t = \frac{1}{0.0283 \angle 8.13^\circ}$$

$$\hookrightarrow 35.335 \angle -8.13^\circ$$

$$pf = \cos(-8.13^\circ) = 0.9899$$

$$pf \cong 99$$

77. A 250 V, 30 Hz generator supplies power to a parallel circuit consisting of a 20 hp motor whose efficiency is 90% at 0.80 lagging and a second load that draws an apparent power of 7 kVA at unity pf. Determine the system power factor.

Solution:

$$P_1 = \frac{P_{out}}{\eta} = \frac{20(746)}{0.9} = 16.58 \text{ kW}$$

$$S_1 = \frac{P_1}{pf} = \frac{16.58}{0.8} = 20.725 \text{ kVA}$$

$$\theta_1 = \cos^{-1} 0.8 = 36.869^\circ$$

$$S_t = S_1 + S_2$$

$$\dot{\iota} 20.725 \angle -36.869^\circ + 7$$

$$\dot{\iota} 23.58 - j 12.434$$

$$S_t = 26.657 \angle -27.803^\circ$$

$$pf_t = \cos 27.803^\circ$$

$$pf_t = 0.884 \text{ lagging}$$

78. A circuit consists of  $X_a = j5$  ohms,  $X_c = -j5$  ohms and  $R = 5$  ohms all are connected in parallel. Find the equivalent impedance.

Solution:

$$\frac{1}{Z_t} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$\frac{1}{Z_t} = \frac{1}{j5} + \frac{1}{-j5} + \frac{1}{5}$$

$$-j0.2 + j0.2 + 0.2 = 0.2$$

$$Z_t = \frac{1}{0.2} = 5\Omega$$

79 A pure capacitance of  $530.515 \times 10^{-6}$  farad and an inductance of  $530.515 \times 10^{-4}$  henry are connected in parallel across an AC power source. Solve for their resultant impedance assuming that the frequency is 30 Hz.

Solution:

$$X_c = -j \frac{1}{2\pi f C} = \frac{1}{2\pi(30)(530.515 \times 10^{-6})} = -j 10$$

$$X_L = j 2\pi f L = j 2\pi(30)(530.515 \times 10^{-4}) = j 10$$

$$\frac{1}{Z_t} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$j \frac{1}{-j 10} + \frac{1}{j 10} = 0$$

$$Z_t = \frac{1}{0}$$

$$Z_t = \text{undefined}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

80. Three impedances  $Z_a, Z_c, Z_r$  are connected in parallel. If at 60 Hz,  $Z_a = 0 + j8$ ,  $Z_c = 0 - j2$  and  $Z_r = 5 + j0$  ohms. Solve for the resultant power factor.

Solution:

$$\frac{1}{Z_t} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$\frac{1}{Z_t} = \frac{1}{j8} + \frac{1}{-j12} + \frac{1}{j5}$$

$$= -j0.125 + j0.5 + 0.2$$

$$= 0.2 + j0.375$$

$$= 0.425 \angle 61.927^\circ$$

$$Z_t = \frac{1}{0.425 \angle 61.927^\circ}$$

$$= 2.353 \angle -61.927^\circ \Omega$$

$$pf = \cos(-61.927)$$

$$pf = 0.47 \text{ leading}$$

81. A capacitor, an electric resistance heater, and an impedance are connected in parallel to a 120 V, 60 Hz system. The capacitor draws 50 VAR, the heater draws 100 W and the impedance coil draws 269 VA at a pf of 0.74 lagging. Determine the system power factor.

Solution:

$$S_1 = j50$$

$$S_2 = 100$$

$$\theta_3 = \cos^{-1} 0.74 = 42.268^\circ$$

$$S_3 = 269 \angle -42.268^\circ = 199.06 - j180.93$$

$$S_t = S_1 + S_2 + S_3 = j50 + 100 + 199.06 - j180.93$$

$$S_t = 299.06 - j130.93 = 326.46 \angle -23.64^\circ \text{ VA}$$

$$pf_t = \cos(-23.64^\circ)$$

$$pf_t = 0.916 \text{ lagging}$$

82. A resistance of 5 ohms is connected in series with a capacitor of 442.1  $\mu\text{F}$ . The combination is then connected in parallel with an inductance of 21.22 mH. Solve for the resultant current if the circuit is connected across a 120 V, 60 Hz AC source.

Solution:

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(60)(442.1 \times 10^{-6})} = 6 \Omega$$

$$Z_1 = R - jX_C = 5 - j6 = 7.8 \angle -50.19^\circ$$

$$Z_2 = j2\pi fL = j(2\pi)(60)(0.02122) = j8$$

$$\frac{1}{Z_t} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{7.81 \angle -50.19^\circ} + \frac{1}{j8}$$

$$\hat{=} 0.128 \angle 5.19^\circ - j0.125$$

$$\hat{=} 0.08195 + j0.0983 - j0.125$$

$$\hat{=} 0.08195 - j0.0267$$

$$\hat{=} 0.08618 \angle 18.046^\circ$$

$$Z_t = \frac{1}{0.08618 \angle 18.046^\circ} = 11.6 \angle -18.046^\circ$$

$$I_t = \frac{E_t}{Z_T} = \frac{120}{11.16} = 10.34 \text{ A}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

83. A circuit consists of  $X_a = j10$  ohms,  $X_c = -j25$  ohms and  $R = 15$  ohms all are connected in parallel. Find the equivalent impedance.

Solution:

$$\frac{1}{Z_t} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$\frac{1}{Z_t} = \frac{1}{j10} + \frac{1}{-j25} + \frac{1}{15}$$

$$= -j0.2 + j0.2 + 0.2 = 0.06$$

$$Z_t = \frac{1}{0.06} = 16.67 \Omega$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

84. Calculate the current in this circuit, and also the amount of mechanical power (in units of "horsepower") required to turn this alternator (assume 100% efficiency): given, volts and 4.6 resistance.

Soloution

$$I = V / R$$

$$I = 480 / 4.6$$

$$I = 104.35 \text{ A}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

85. The power factor for the circuit, overall, has been substantially improved. The main current has been decreased from 1.41 amps to 994.7 milliamps, while the power dissipated at the load resistor remains unchanged at 119.365 watts. The power factor is much closer to being 1:

Solution:

p.f. = true power / apparent power

p.f. = 119.365W / 119.366 VA

p.f. = 0.9999887

impedance (polar) angle = 0.272

$\cos 0.272 = 0.9999887$

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

86. A 250 V, 30 Hz generator supplies power to a parallel circuit consisting of a 20 hp motor whose efficiency is 80% at 0.70 lagging and a second load that draws an apparent power of 7 kVA at unity pf. Determine the system power factor.

Solution:

$$P_1 = \frac{P_{out}}{\eta} = \frac{20(746)}{0.8} = 18.65 \text{ kW}$$

$$S_1 = \frac{P_1}{pf} = \frac{18.65}{0.7} = 26.64 \text{ kVA}$$

$$\theta_1 = \cos^{-1} 0.7 = 45.57^\circ$$

$$S_t = S_1 + S_2$$

$$\hookrightarrow 26.64 \angle -45.57^\circ + 7$$

$$\hookrightarrow 26.64 - j 19.023$$

$$S_t = 31.93 \angle -36.56^\circ$$

$$pf_t = \cos 36.56^\circ$$

$$pf_t = 0.803 \text{ lagging}$$

87. An inductive reactance of  $20\Omega$  is connected in parallel with capacitive reactance of  $50\Omega$ . If the combination is connected in series with  $10\Omega$  resistance, solve for the total impedance of the circuit.

Solution:

$$z_T = \left[ \frac{1}{0+jX_L} + \frac{1}{0-jX_C} \right]^{-1} + 10$$

$$Z_T = \left[ -j\frac{1}{X_L} + j\frac{1}{X_C} \right]^{-1} + 10$$

$$Z_T = \left[ -j\frac{1}{20} + j\frac{1}{50} \right]^{-1} + 10$$

$$Z_T = 10 + j33.33$$

$$Z_T = 34.80 \angle 73.30$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

88. A given load takes 50kVa at 0.8 lagging power factor while another load connected in parallel across the same source takes 70 kVa at 0.65 lagging power factor. Find the total apparent power.

Solution:

$$S_1 = 50 \text{ kVa @ } 0.8 \text{ lagging}$$

$$S_2 = 70 \text{ kVa @ } 0.65 \text{ lagging}$$

$$S_T = S_1 + S_2$$

$$S_T = 50 \angle -\cos^{-1} 0.8 + 70 \angle -\cos^{-1} 0.65$$

$$S_T = 50 \angle -36.87 + 80 \angle -49.46$$

$$S_T = 92 - 90.80j^\circ \text{ kVa}$$

89. Given:  $V = 50 \angle 30^\circ$ ;  $I_T = 27.9 \angle 57.8^\circ$  A. Determine the value of  $Z_1$ .

Solution:

$$Z_{ab} = (Z_2 \times Z_3) / (Z_2 + Z_3)$$

$$Z_{ab} = (4 - j4) \times (20) / (4 - j4) + (20)$$

$$Z_{ab} = 4.65 \angle -35.54^\circ \Omega$$

$$I'' = V / Z_{ab}$$

$$I'' = (100 \angle 90^\circ) / (4.65 \angle -35.54^\circ \Omega)$$

$$I'' = -12.5 + j17.5 \text{ A}$$

$$I' = I_T - I''$$

$$I' = (-10.86 + j49) - (-12.5 + j17.5)$$

$$I' = 31.54 \angle 87.02^\circ \text{ A}$$

$$Z = V / I'$$

$$Z = (100 \angle 90^\circ) / (31.54 \angle 87.02^\circ)$$

$$Z = 3.17 \angle 2.98^\circ \Omega$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

90. An inductive reactance of  $20\Omega$  is connected in parallel with capacitive reactance of  $50\Omega$ . If the combination is connected in series with  $20\Omega$  resistance, solve for the total impedance of the circuit.

Solution:

$$z_T = \left[ \frac{1}{0+jX_L} + \frac{1}{0-jX_L} \right]^{-1} + 25$$

$$Z_T = \left[ -j\frac{1}{X_L} + j\frac{1}{X_C} \right]^{-1} + 25$$

$$Z_T = \left[ -j\frac{1}{50} + j\frac{1}{20} \right]^{-1} + 25$$

$$Z_T = j30 + 25$$

$$Z_T = 25 - 33.333j$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

91. A two-element series circuit with  $R = 10 \Omega$  and  $X_L = 25\Omega$  has an effective voltage of 110 volt across the resistor. Find the complex power and the power factor.

Given:

$$R = 10 \Omega$$

$$X_L = 25 \Omega$$

$$E_R = 110V$$

Solution:

$$I = V_R / R$$

$$I = 110 / 10$$

$$I = 11 A$$

$$P_R = I^2 R$$

$$P_R = (11)^2 (10)$$

$$P_R = 1210 W$$

$$Q_L = I^2 X_L$$

$$Q_L = (11)^2 (15)$$

$$Q_L = 1815 \text{ VARS}$$

$$\text{Complex Power} = 1210 + j1815$$

$$\text{Power Factor} = P / S$$

$$\text{Power Factor} = 1210 / \sqrt{(1210)^2 + (1815)^2}$$

$$\text{Power Factor} = 0.56 \text{ lagging}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

92. A two element series circuit has average power of 760W and a power factor of 0.8 leading. Determine the circuit elements if the applied voltage  $V = 66.0 \cos(6000t + 30^\circ)$  V.

Given:

$$P_{ave} = 760 \text{ W} ; \text{ p.f} = 0.8$$

Solution:

$$E_{Effective} = 66.0 / \sqrt{2} = 46.67$$

$$P = V_{eff} \times I_{eff} \cos \theta$$

$$I_{eff} = 760 / [(70)(0.8)]$$

$$I_{eff} = 13.57 \text{ A}$$

$$I_{eff}^2 R = 760$$

$$R = 760 / 19^2$$

$$R = 2.11 \Omega$$

For leading power factor ,

$$\theta = \cos^{-1}(0.8)$$

$$\theta = 36.87^\circ$$

$$z = R - jX_C ; X_C = 2.11 \tan 36.87^\circ$$

Therefore,

$$2.11 = 1 / \omega C$$

$$C = 1 / [(2.11)(2\pi)(60)]$$

$$C = 1.25 \text{ } \mu\text{ F}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

93. A two branch parallel circuit has a corresponding phasor diagram as shown below. Find the branch impedances  $Z_1$  and  $Z_2$ .

Solution using  $V_1$  as reference phasor

$$I_1 = 5.2 \angle -75.5^\circ \text{ A}; I_2 = 8.21 \angle 90^\circ \text{ A}$$

$$Z_1 = V/I_1$$

$$Z_1 = (100 \angle 0^\circ) / (5.2 \angle -75.5^\circ)$$

$$Z_1 = 20.2 \angle 82.87^\circ$$

$$Z_1 = 4.82 + j18.62 \Omega$$

$$R_1 = 4.82 \Omega$$

$$X_{L1} = 18.62 \Omega$$

$$Z_2 = V/I_2$$

$$Z_2 = (100 \angle 0^\circ) / (8.21 \angle 90^\circ)$$

$$Z_2 = 15 \angle -90^\circ \Omega$$

$$Z_2 = 0 - j12.18 \Omega$$

$$R_2 = 0 \Omega$$

$$X_{C2} = 12.18 \Omega$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

94. A two branch parallel circuit has an applied voltage and resulting currents as given in the phasordigram shown in the figure. Find the branch impedances  $Z_1$  and  $Z_2$ .

Given:

$$I_1 = 15A$$

$$I_2 = 13A$$

$$V = 220V$$

Solution:

Using X as reference phasor

$$V_1 = 220 \angle -30^\circ$$

$$I_1 = 15 \angle 30^\circ$$

$$I_2 = 13 \angle -53.1^\circ$$

$$Z_1 = V / I_1$$

$$Z_1 = (220 \angle -30^\circ) / (15 \angle 30^\circ)$$

$$Z_1 = 14.67 \angle -60^\circ$$

$$Z_1 = 7.33 - j12.70\Omega$$

$$Z_2 = V / I_2$$

$$Z_2 = (220 \angle -30^\circ) / (13 \angle -53.1^\circ)$$

$$Z_2 = 16.92 \angle 23.1^\circ$$

$$Z_2 = 15.576 + j6.64\Omega$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

95. A resistor of 10 ohms and an impedance of  $30 + j6$  ohms are connected in parallel across a 220 volts supply. What is the power factor of the load?

Solution:

$$\frac{1}{Z_t} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{10} + \frac{1}{30 + j6}$$

$$\hat{i} 0.1 + \frac{1}{0.033 \angle -11.31^\circ}$$

$$\hat{i} 0.1 + 0.00894 \angle -26.565^\circ$$

$$\hat{i} 0.02 + 0.0321 - j6.410 \times 10^{-3}$$

$$\hat{i} 0.0524 \angle -7.014^\circ$$

$$Z_t = \frac{1}{0.0524 \angle -7.014^\circ}$$

$$\hat{i} 19.05 \angle 7.014^\circ$$

$$pf = \cos(7.014^\circ) = 0.9925$$

$$pf \cong 99.25$$

96. A circuit consists of  $X_a = j10$  ohms,  $X_c = -j10$  ohms and  $R = 30$  ohms all are connected in parallel. Find the equivalent impedance.

Solution:

$$\frac{1}{Z_t} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$\frac{1}{Z_t} = \frac{1}{j10} + \frac{1}{-j10} + \frac{1}{30}$$

$$\therefore j0.1 - j0.1 + 0.03 = 0.03$$

$$Z_t = \frac{1}{0.03} = 33.33 \Omega$$

97. Given  $I_1 = 4 \angle -45^\circ$  and  $I_T = 5.21 \angle 37.4^\circ$  A. Find  $Z_2$

Solution:

$$I_2 = I_T - I_1$$

$$I_2 = (5.21 \angle 37.4^\circ) - (4 \angle -45^\circ)$$

$$I_2 = 1.31 + j6.00$$

$$I_2 = 6.12 \angle 77.67^\circ$$

$$I_1 Z_1 = I_2 Z_2$$

$$Z_2 = (I_1 Z_1) / I_2$$

$$Z_2 = [(4 \angle -45^\circ)(5)] / (6.12 \angle 77.67^\circ)$$

$$Z_2 = -1.76 - j2.75 \Omega$$

Group IV

June

EE 3303

Engr. Kenneth F. Fajilan

98. A coil of a 100-ohm resistance and of 50 mH inductance is connected in parallel with a  $4.7 \mu\text{F}$  capacitor. What is the power factor of the circuit?

Solution:

$$X_L = \omega L = 377(0.05) = 18.85 \Omega$$

$$X_c = \frac{1}{\omega C} = \frac{1}{377(4.7 \times 10^{-6})} = 564.3659 \Omega$$

$$\frac{1}{Z_t} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{100 + j18.85} + \frac{1}{-j564.3659}$$

$$= \frac{1}{101.7611 \angle 10.6749^\circ} = j0.00177$$

$$= 0.01030 \angle -20.3946^\circ$$

$$Z_t = \frac{1}{0.01030 \angle -20.3946^\circ}$$

$$= 97.06197 \angle 20.3946^\circ$$

$$pf = \cos(20.3946^\circ)$$

$$pf \cong 0.94$$

Group IV

June

EE 3303

Engr. Kenneth F. Fajilan

99. Three impedances  $Z_a, Z_c, Z_r$  are connected in parallel. If at 60 Hz,  $Z_a = 0 + j15$ ,  $Z_c = 0 - j25$  and  $Z_r = 9 + j0$  ohms. Solve for the resultant power factor.

Solution:

$$\frac{1}{Z_t} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$\frac{1}{Z_t} = \frac{1}{j15} + \frac{1}{-j25} + \frac{1}{9}$$

$$= -j0.0667 + j0.04 + 0.11$$

$$= 0.11 - j0.02667$$

$$= 0.2885 \angle -67.5864^\circ$$

$$Z_t = \frac{1}{0.2885 \angle -67.5864^\circ}$$

$$= 3.4662 \angle 67.8564^\circ \Omega$$

$$pf = \cos(67.8564)$$

$$pf = 0.3769 \text{ leading}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

100. A voltmeter placed across the 3 ohms resistor shown, if the voltmeter reads 30 volts. What is the ammeter reading?

Solution:

$$I_{3\Omega} = 30 / 3 = 10A$$

$$R_{bc} = (5 \times 2) / (5 + 2) = 1.43\Omega$$

$$Z_1 = R_{ab} + 10$$

$$Z_1 = 1.43 + 10$$

$$Z_1 = 11.43\Omega$$

$$Z_{eq} = (Z_1 Z_2) / (Z_1 + Z_2)$$

$$Z_{eq} = (1.43)(3 + j3) / (1.43 + 3 + j3)$$

$$Z_{eq} = 3.28 \angle -33.25^\circ$$

$$I_{ac} = (15)(3 + j3) / 11.43$$

$$I_{ac} = 3.92 + j3.92$$

Ammeter Reading

$$I_{am} = I_{3\Omega} + I_{ac}$$

$$I_{am} = 10 + (3.92 + j3.92)$$

$$I_{am} = 14.46 \angle 15.73^\circ$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

101. A series combination of R and C is in parallel with a 20Ω resistor. A 60 Hz source resulting in a total current of 7.21A, a current through the 20Ω resistor is 5A and the current in the RC branch is 3.3A. Determine the R and C.

Solution:

$$\theta = \cos^{-1} [(I_T^2 - I_R^2 - I_Z^2)] / (2I_R I_Z)$$

$$\theta = \cos^{-1} [(7.21^2 - 5^2 - 3.3^2)] / (5)(7.1) \quad (3.3)$$

$$\theta = 82.10^\circ$$

$$V_T = (20\Omega)(5A)$$

$$V = 100V$$

$$Z = V_T / I_Z$$

$$Z = 100V / 3.3A$$

$$Z = 30.30 \angle \theta \quad \Omega$$

$$Z = 30.30 \angle 82.10^\circ \quad \Omega$$

$$Z = 4.16 + j 30.01$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

102. A load of 300kW with a power factor of 0.7 lagging has the power factor improved to 0.80 lagging by the addition of parallel capacitors. What kVAR of capacitors does require to improved the power factor?

Given:

$$P = 300\text{kW}$$

$$P_{f_i} = 0.70 \text{ lagging}$$

$$P_{f_f} = 0.80 \text{ lagging}$$

Solution:

$$\theta_i = \cos^{-1} 0.70$$

$$\theta_i = 45.57^\circ$$

$$\theta_f = \cos^{-1} 0.80$$

$$\theta_f = 36.87^\circ$$

$$Q_{\text{req}} = P [\tan \theta_i - \tan \theta_f]$$

$$Q_{\text{req}} = 300\text{kW} (\tan 45.57^\circ - \tan 36.87^\circ)$$

$$Q_{\text{req}} = 810.28\text{kVAR (leading)}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

103. A 30 ohm resistor is connected in series with a parallel combination of a capacitance C and 15mH pure inductance. At angular frequency  $\omega = 1000\text{rad/s}$ , find C such that the line current is  $45^\circ$  out of phase with the line voltage.

Given:

$$R = 30\Omega$$

$$L = 15\text{mH}$$

$$\omega = 1000\text{rad/s}$$

$$C = ?$$

Solution:

$$Z = R \pm jX$$

$$Z_T = 30 + [(j15)(-jX_C)] / (15 - X_C) j$$

$$Z_T = \infty$$

$$0 = 30 + [(j15)(-jX_C)] / (15 - X_C) j$$

$$X_C = 60\Omega$$

$$C = 1 / (2 \pi f X_C)$$

$$C = 1 / [(1000)(60)]$$

$$C = 16.6667 \mu\text{F}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

104. An inductive coil consumes 600W of power at 11A and 110V and 60Hz. Determine the resistance and the inductance of the coil.

Given:

$$P = 600\text{W}$$

$$I = 11\text{A}$$

Solution:

$$P_T = V_T I_T \cos \theta$$

$$\theta = \cos^{-1} [(110 \times 11) / 600]$$

$$\theta = 60.27^\circ$$

$$Z_T = V_T / I_T$$

$$Z_T = 110 / 11$$

$$Z_T = 10\Omega$$

$$Z_T = 10 \angle 60.27^\circ$$

$$Z_T = 32.5 + j9.53$$

$$X_L = 9.53$$

$$X_L = 2 \pi fL$$

$$X_L = 9.53$$

$$L = 9.53 / (2 \pi)(60)$$

$$L = 25.2700\text{mH}$$

$$R = 5\Omega$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

105. An inductive coil having a 20 ohm resistance and unknown reactance is connected in parallel with 120 ohm resistor. The combination is connected across a 110V 50/  $\pi$  Hz source. If the power delivered by the source is 400W, find the value of the inductance.

Solution;

$$P_T = P_1 + P_2$$

$$P_T = (I_1^2 R) + (V^2/R)$$

$$400 = (I_1^2 (20)) + (110^2/120)$$

$$I_1 = 3.8676 \text{ A}$$

$$Z = V_2 / I_2$$

$$Z = 110 / 3.8676$$

$$Z = 28.44 \Omega$$

$$Z^2 = R^2 + X^2$$

$$(28.44)^2 = 20^2 + X^2$$

$$X_L = 20.22$$

$$X_L = 2 \pi fL$$

$$L = 20.22 / (2 \pi)(50 / \pi)$$

$$L = 0.2022 \text{ H}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

106. A given load takes 40kVa at 0.6 lagging power factor while another load connected in parallel across the same source takes 80 kVa at 0.7 lagging power factor. Find the total apparent power.

Solution:

$$S_1 = 40 \text{ kVa @ } 0.6 \text{ lagging}$$

$$S_2 = 80 \text{ kVa @ } 0.7 \text{ lagging}$$

$$S_T = S_1 + S_2$$

$$S_T = 40 \angle \cos^{-1} 0.6 + 80 \angle \cos^{-1} 0.7$$

$$S_T = 40 \angle -53.13 + 80 \angle -45.57$$

$$S_T = 80.00 - j89.13^\circ \text{ kVa}$$

107. A parallel circuit consists of a resistor having a conductance of 5 mhos, an inductive reactor having a susceptance of 9 mhos and a capacitive reactor having a susceptance of 7 mhos. What is the impedance of the circuit?

Solution:

$$G_T = 5\Omega$$

$$\beta_{TL} = 9\Omega$$

$$\beta_{TC} = 7\Omega$$

$$Y_T = 5 - j9 + j7$$

$$Y_T = 4 - j2$$

$$Z_T = \frac{1}{4 - j2}$$

$$Z_T = 0.2236 \angle 26.57^\circ$$

108. Two parallel branches have admittances of  $5+j2$  and  $3-j4$  respectively. If the current in the first branch is  $12\text{ A}$ , determine the total current supplied to the combination.

Solution:

$$Y_T = Y_1 + Y_2$$

$$Y_T = 5 + j2 + 3 - j4$$

$$Y_T = 8 - j2$$

$$Z_1 = 8.25 \angle -14.04^\circ$$

$$E = IZ$$

$$E = (12)(8.25 \angle -14.04^\circ)$$

$$E = 98.95 \angle -14.04^\circ$$

$$Y_T = 8.25 \angle -14.04^\circ$$

$$I_T = E X_T$$

$$98.95 \angle -14.04^\circ \quad \parallel \quad 8.25 \angle -14.04^\circ \angle$$

$$I_T = \angle$$

$$I_T = 11.2178 \angle 64.44^\circ$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

109. An inductive coil with a resistance R and inductance L is connected in parallel with a 30 Ω resistor. The combination is then connected across a 60 Hz source. If the currents in the coil, resistor and total are 7,4 and 5 A respectively. Determine the inductance of the coil.

Solution:

$$E = (30)(4)$$

$$E = 120 \text{ V}$$

$$\beta = \cos^{-1} \left[ \frac{7^2 + 4^2 - 5^2}{(7)(5)(4)} \right]$$

$$\beta = 74.40^\circ$$

$$\theta = 180 - \beta$$

$$\theta = 106.60^\circ$$

$$I = \frac{E}{Z}; Z = \frac{120}{5} = 24 \Omega$$

$$Z = 24 \angle 74.40^\circ$$

$$Z = 6.45 + j 23.12$$

$$R = 6.45 \Omega$$

$$X_L = 23.12 \Omega$$

$$L = \frac{23.12}{(2\pi)(60)}$$

$$L = 0.06 \text{ H}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

110. The power factor for the circuit, overall, has been substantially improved. The main current has been decreased from 1.41 amps to 994.7 milliamps, while the power dissipated at the load resistor remains unchanged at 111.782 watts. The power factor is much closer to being 1:

Solution:

P.f. = true power / apparent power

P.f. = 111.782W / 111.982 VA

P.f. = 0.99821

impedance (polar) angle = 3.4286

$\cos 3.4286 = 0.99821$

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

111. Calculate the current in this circuit, and also the amount of mechanical power (in units of "horsepower") required to turn this alternator (assume 100% efficiency): given, volts and 5.6 resistance.

Solution:

$$I = V / R$$

$$I = 480 / 5.6$$

$$I = 85.71 \text{ A}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

112. A load of  $10 + j15$  is connected across a 220 volts source. Determine the power factor and the VARS.

Solution:

$$Z = 10 + j15 = 18.03 \angle 56.31^\circ$$
$$\text{pf} = \cos \Theta = \cos 56.31^\circ = 0.55$$

$$\text{pf} = 55 \%$$

$$Q = EI \sin \Theta = \frac{E^2}{Z} \sin \Theta = \frac{220^2}{18.03} \sin 56.31^\circ$$

$$Q = 2233.57 \text{ VARS}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

113. The network is part of the schematic describing an industrial electronic sensing device. What is the total impedance of the circuit at 5 kHz?

Solution:

$$Z_1 = 50 + 1/j\omega C = 50 + 1/(2\pi)(2 \times 10^3)(5 \times 10^{-6}) \\ = 50 - j15.92$$

$$Z_2 = 80 + j\omega L = j(2\pi)(2 \times 10^3)(5 \times 10^{-6}) \\ = 80 + j.06$$

$$Z_3 = 100$$

$$1/Z = 1/Z_1 + 1/Z_2 + 1/Z_3$$

$$1/Z = 10^{-3} (10 + j15.92 + j9.745 + 3.605 - j.06)$$

$$Z = (13.605 + j25.605) \times 10^{-3} \\ = 26.17 \times 10^{-3} \angle 8.97^\circ$$

$$Z = 28.995 \angle 62.02^\circ \Omega$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

114. Two electric units are connected across a source whose frequency is 50 cps. If the voltage drop across the units are 120 and 95 volts and they are out of phase by  $90^\circ$ , what is the equation of the voltage across the source?

Solution:

$$E_T = \sqrt{E_1^2 + E_2^2}$$
$$= \sqrt{120^2 + 95^2}$$

$$E_T = 5 \sqrt{937} = 153.05$$

$$\Theta = \tan^{-1} \left( \frac{95}{120} \right)$$

$$\Theta = 38.37^\circ$$

$$E_{Mt} = E_T \sqrt{2}$$
$$= 153.05 \left( \sqrt{2} \right)$$

$$E_{Mt} = 216.45 \text{ V}$$

$$\omega = 2\pi f$$

$$= 2\pi (50)$$

$$\omega = 314$$

$$E_t = 216.45 \sin (314t + 38.37^\circ) \text{ V}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

115. An impedance draws a current of 12 A at 0.8 lagging power factor from a source voltage of 240V, 60 Hz. What is the current when resistance is reduced by 50%?

Solution:

$$Z = \frac{e}{i} = \frac{240}{12} = 20\Omega$$

$$\text{Pf} = \frac{R}{Z}$$

$$R = Z (\text{Pf}) = (20) (0.8) = 16\Omega$$

$$X_L = \sqrt{Z^2 - R^2}$$

$$= \sqrt{20^2 - 16^2}$$

$$X_L = 12\Omega$$

When  $R = 8\Omega$

$$Z = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{8^2 + 12^2}$$

$$Z = 2\sqrt{13} \Omega$$

$$I = \frac{e}{z} = Z = \frac{240 V}{2\sqrt{13}\Omega}$$

$$I = 45.36 \text{ A}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

116. A current of 20 A and a power factor of 0.7 lagging is taken from a single phase 240 volt supply. The reactive power of the system is?

Solution:

$$\theta = \cos^{-1} 0.7 = 45.58^\circ$$

$$Q = EI \sin \theta$$

$$Q = (240)(20) \sin 45.58^\circ$$

$$Q = 3428.29 \text{ VARS}$$

117. A coil of 50-ohm resistance and of 150 mH inductance is connected in parallel with a 60  $\mu$ F capacitor. What is the power factor of the circuit?

Solution:

$$X_L = \omega L = (377) (0.15) = 56.55 \Omega$$

$$X_C = 1 / \omega C = 1 / (377) (60 \times 10^{-6}) = 44.21 \Omega$$

$$(1 / Z_T) = (1 / Z_1) + (1 / Z_2) = [1 / (50 + j56.55)] + (1 / -j44.21)$$

$$(1 / Z_T) = [1 / (0.0125 \text{ cjs } 45.744^\circ)]$$

$$Z_T = 36.85 \text{ cjs } -53.30^\circ \Omega$$

$$\text{Pf} = \cos -53.30^\circ$$

o

$$\text{Pf} = 0.6$$

118. A current of 10 A and a power factor of 0.7 lagging is taken from a single phase 110 volt supply. The reactive power of the system is?

Solution:

$$\theta = \cos^{-1} 0.7 = 45.53^\circ$$

$$Q = E I \sin \theta$$

$$Q = (110)(10)\sin 45.53^\circ$$

$$Q = 784.98 \text{ VARS}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

119. A capacitor of 3.19 microfarad is connected in parallel with a resistance of 2,000 ohms. The combination inductance 795 mH and a resistance of 100 ohms across a supply given by  $e = 400\sin(314t + 60^\circ)$   
 Determine the instantaneous equation for the current and its 314 rms value.

$$X_L = \omega L = 314 (795 \text{ mH}) = 250 \text{ ohms}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{314(3.18 \text{ microfarad})}$$

$$Z_T = 100 + j250 + \frac{2,000(-j1,000)}{2,000 - j1,000} = 500 - j550$$

For the third harmonics:

$$X_L = 3 \omega L = 3 \times 314 (795 \text{ mH}) = 750 \text{ ohms}$$

$$Z_T = 100 + j750 + \frac{2000(-j333.333)}{2000 - j333.333} = 452 \angle 7^\circ 0.105 \text{ ohms}$$

$$I = 0.53814 \sin(314t + 47.726^\circ) + 0.029053 \sin(942t - 0.105^\circ) \text{ amperes}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

120. A single phase load on 220 V takes a 35kW at 0.60 lagging .Find the kVAR size of capacitor , which maybe connected in parallel with this motor to bring the resultant power factor to 1.0.

$$\theta = \frac{1}{\cos} (0.60) = 53.13^\circ$$

$$Q_L = P_L \tan \theta_L = 35 \tan 53.13$$

$$= 47 \text{ kVAR}$$

121. An inductive reactance of 10 ohms is connected in parallel with a capacitive reactance of 30 ohms. If the combination is connected in series with a 10 ohms resistance. Solve for the equivalent power factor of the combination.

SOLUTION :

$$Z_1 = 10 + \frac{(J10)(-J20)}{(J10+J30)}$$

$$Z_1 = 10 + \frac{-j^2(200)}{-j20} = 10+j15$$

$$Z_1 = 9.999+14.99i$$

$$\text{Pf} = \cos 56.31$$

$$\text{Pf} = 0.555 \text{ lagging}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

122. Given three impedances:  $Z_1 = 10+j0$ ,  $Z_2 = 3+j4$ ,  $Z_3 = 8-j6$ . Impedance  $Z_2$  and  $Z_3$  are connected in parallel and the combination is connected in series with impedance  $Z_1$ , across 120 V single phase 60 Hz source. Find the total power drawn by the impedances.

SOLUTION :

$$Z_1 = 10+j0$$

$$Z_2 = 3+j4$$

$$Z_3 = 8-j6$$

$$Z_T = 10 + \frac{3+j4(8-j6)}{(3+j4)+(8-j6)}$$

$$= 10+4+j2$$

$$P = \frac{120^2}{14.142} \cos (8.13 \text{ degree})$$

$$P = 1008 \text{ watts}$$

123. Has a power of 180 Watts and a power factor of 0.8 lagging. Find the circuit constants.

Given:

$$i = 3.52 \sin (5000t + 45^\circ) \text{ A}$$

$$P = 180 \text{ W}$$

$$\cos \theta = 0.8$$

Solution:

$$\text{The effective value of current} = (3.52) / \sqrt{2} = 2.5 \text{ A}$$

$$P = I^2 R$$

$$R = (180) / (2.5)^2$$

$$\text{Impedance angle } \theta = \cos^{-1} 0.8 = 36.87^\circ$$

Number 2 element is an inductor, using power triangle,

$$(Q / P) = \tan 36.87^\circ = [(I_{\text{eff}})^2 (X_L)] / 180$$

$$X_L = (180 \tan 36.87^\circ) / 2.5^2$$

$$X_L = 21.6 \Omega$$

Since  $X_L = 2 \pi f L$

$$\omega = 2 \pi f = 5000$$

$$21.6 = 5000L$$

$$L = 21.6 / 5000$$

$$L = 4.32 \text{ mH}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

1. 124. A 3phase feeder carries two balanced loads . The power observed by each is measured by two wattmeter method giving the following readings:

$$\text{First load : } W_1 = 96 \text{ kN ; } W_2 = 160 \text{ kW}$$

$$\text{Second load : } W_1 = 90 \text{ kN ; } W_2 = 48 \text{ kW}$$

What is the combined load on the feeder and the power factor ?

Solution:

$$\begin{aligned} P_T &= P_1 + P_2 = (W_1 + W_2) \cos \theta \\ &= (96 + 160) + (90 + 48) \\ &= 394 \text{ K w} \end{aligned}$$

Power factor of each load:

First Load:  $w_1 = 96 \text{ kN}$ ;  $W_2 = 160 \text{ kW}$

$$\begin{aligned} Q_1 &= (w_1 + w_2) \tan \theta \\ &= (96 + 160) (0.433) \\ &= 110.85 \text{ kVar} \end{aligned}$$

$$\begin{aligned} \text{When both loads are lagging p.f.} &= \cos \left( \arctan \frac{110.85 + 72.7}{394} \right) \\ &= 0.906 \text{ lagging} \end{aligned}$$

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan

125. A current of 10A and a power factor of 0.8 lagging is taken from a single phase 250 V supply. The reactive power of the system is :

SOLUTION :

$$\theta = \cos^{-1} 0.8 = 36.869 \text{ degree}$$

$$Q = EI \sin \theta$$

$$Q = (250 \times 10) \sin 36.869 \text{ degree}$$

$$Q = 1500 \text{ VARS}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

126. A total current of 10 A flows through the parallel combination of three impedance : (2-j5)ohms, (6+j3) ohms and (3+j4) ohms. Calculate the current flowing through each branch. Find also the power factor of the combination.

SOLUTION :

$$\text{Let } Z_1 = (2-j5), \quad Z_2 = (6+j3), \quad Z_3 = (3+j4)$$

$$Z_1 Z_2 = (2-j5)(6+j3) = 27-j24, \quad Z_2 Z_3 = (6+j3)(3+j4) = 6+j33$$

$$Z_3 Z_1 = (3+j4)(2-j5) = 26-j7 : \quad Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1 = 59+j2$$

Now,

$$I_1 = (10+j0) \times \frac{6+j33}{59+j2} = 1.21+j5.55$$

$$I_2 = (10+j0) \times \frac{26+j7}{59+j2} = 4.36-j1.33$$

$$I_3 = (10+j0) \times \frac{27-j24}{59+j2} = 4.43 -j4.22$$

$$Z = \frac{(2-j5)(6+j33)}{59+j2} = 3.01 + j 0.51$$

$$V = 10 \times (3.007+0.5086i) = 30.07+5.08i$$

Combination power factor :

$$\text{Cos } 9.6 = 0.986 \text{ (lagging)}$$

127. A single phase inductive load takes 70kVA at 0.60 p.f. lagging . Solve for the kVAR of a capacitor required to improve the power factor to 1.0.

$$\theta = \frac{1}{\cos} (0.60) = 53.13$$

$$Q_L = S_L \sin \theta_L = 70 \sin 45^\circ$$

$$= 50\text{kVAR}$$

128. A single phase load on 220 V takes a 5kW at 0.60 lagging .Find the kVAR size of capacitor , which maybe connected in parallel with this motor to bring the resultant power factor to 1.0.

$$\theta = \frac{1}{\cos} (0.60) = 53.13^\circ$$

$$Q_L = P_L \tan \theta_L = 5 \tan 53.13$$

$$= 6.67 \text{ kVAR}$$

129. A single phase inductive load takes 50 kVA at 0.60 p.f. lagging . Solve for the kVAR of a capacitor required to improve the power factor to 1.0.

$$\theta = \frac{1}{\cos} (0.60) = 53.13^\circ$$

$$Q_L = S_L \sin \theta_L = 50 \sin 45^\circ$$

$$= 40 \text{ kVAR}$$

130. A 140 Kva transformer bank will serve a load expected to draw 120 KW At 0.70 lagging power factor. Solve for the size of the capacitor bank with needed to be acted in order to prevent overloading of the transformer bank

SOLUTION:

$$\theta_1 = \cos^{-1} 0.7 = 45.58 \text{ degree}$$

$$Q_T = \sqrt{S^2 - P^2} = \sqrt{140^2 - 120^2}$$

$$= 72.11 \text{ Kvar}$$

$$Q_C = Q_L - Q_T$$

$$= P_L \tan \theta - Q_T = 120 \tan 45.58 \text{ degree} - 72.11$$

$$Q_C = 50.34 \text{ kVAR}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

131. A short, 3 phase, 3 wire transmission line has a receiving end voltage of 4160 V phase neutral and serving a balanced 3 phase load of 876, 400 volt-amperes at 0.75 p.f lagging . At the receiving end the voltage is 4600V, phase to Neutral and the p.f is 0.9 . solve for the size in kVAR of a capacitor needed to improve the receiving end pf to 0.9 lagging maintaining 4160V.

$$\theta_L = \frac{1}{\cos} (0.75) = 41.41^\circ$$

$$\theta_T = \frac{1}{\cos} (0.9) = 25.84^\circ$$

$$P_L = (876) (0.75) = 657 \text{ kW}$$

$$Q_T = Q_L - Q_C$$

$$= (657) (\tan 41.41 - \tan 25.84)$$

$$= 569.63 \text{ kVAR}$$

132. A three phase, 3 wire transmission line has an impedance per wire of  $3+j7$  ohms, the receiving end load is 1950 KW, 0.65 pf lagging with the line voltage of 13,200 V. Determine the kVAR of the capacitor to be connected at the receiving end to make the pf at that end to 0.8 lagging.

SOLUTION :

$$\theta_l = \cos^{-1} 0.65 = 49.458 \text{ degree}$$

$$\theta_t = \cos^{-1} 0.8 = 36.869 \text{ degree}$$

$$Q_L = P_L \tan \theta = 1950 \tan 49.458 \text{ degree} = 2279.77 \text{ KVAR}$$

$$Q_T = 1950 \tan 36.869 \text{ degree} = 1462.45 \text{ KVAR}$$

$$Q_C = 2279.77 - 1462.45$$

$$Q_C = 817.32 \text{ KVAR}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

133. A 3-phase , 3 wire, short transmission line has a resistance of 3 ohms and a reactance of 8 ohms per wire. At the receiving end, a balanced 3-phase load draws a line current of 60 A, at 13500 V line to line, 0.90 power factor lagging. Assuming the receiving end voltage is maintained at 13,500 V, solve the size in kVAR of capacitors needed to raise the power factor at the receiving end to 0.95 leading.

SOLUTION :

$$P_R = \sqrt{3} \ E I \text{pf}$$

$$P_R = \sqrt{3} \ (13,500)(60)(0.9)$$

$$= 1262.655 \text{ kW}$$

$$\theta = \cos^{-1} 0.9 = 25.84 \text{ lagging}$$

$$\theta_t = \cos^{-1} 0.95 = 18.195 \text{ degree}$$

$$Q_C = Q_R + Q_T$$

$$= 1262.655 \tan 25.84 \text{ degree} + 1262.655 \tan 18.195 \text{ degree}$$

$$Q_C = 1026.505 \text{ kVAR}$$

134. A 1600 watt 230 volt single phase drill with a 45.7 degrees lagging (0.6984) current of 14 amps where given. Find firstly impedance triangle values from these values and then power triangle values.

Find values for improved power factor of 18.2 degrees lagging (0.95) and capacitor required for improved var.

$$Z = \frac{V}{I} \quad z = 230/14 = 16.43\Omega$$

$$R = 16.43 * 0.6984 = 11.475\Omega$$

$$X_L = \sqrt{(16.43^2 - 11.475^2)} = 11.759\Omega$$

$$z_{95} = 11.475 / 0.95 = 12.079\Omega$$

$$x = \sqrt{(12.079^2 - 11.475^2)} = 3.772\Omega$$

$$x_c = 11.759 - 3.772 = 7.987\Omega$$

$$C = 1 / \omega x_c = 1 / (2 * 3.14 * 50 * 7.987) = 0.0003985 = 398.5\mu F$$

Frequency was calculated as 50 Hz.

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

135. A 100  $\Omega$  resistor, a 0.0200 H inductor and a 1.20  $\mu\text{F}$  capacitor are connected in parallel with a circuit made up of a 110  $\Omega$  resistor in series with a 2.40  $\mu\text{F}$  capacitor. A supply of 150 V, 60 Hz is connected to the circuit. Calculate the total current taken from the supply and its phase angle.

For  $Z_1$  (the upper part of the circuit), we have:

$$X_L = 2\pi fL = 2\pi (60)(0.0200) = 7.540 \Omega$$

$$X_C = 12\pi(60)(1.20 \times 10^{-6}) = 2210.485 \Omega$$

$$Z_1 = R_1 + j(X_L - X_C)$$

$$= 100 + j(7.540 - 2210.485)$$

$$= 100 - 2202.9j$$

$$= 2205.21 \angle -87.40^\circ \Omega$$

For  $Z_2$  (the lower part of the circuit), we have:

$$X_C = 12\pi(60)(2.40 \times 10^{-6}) = 1105.243 \Omega$$

$$Z_2 = R_2 + j(X_L - X_C)$$

$$= 110 + j(-1105.243)$$

$$= 1110.7 \angle -84.32^\circ \Omega$$

So the **total impedance**,  $Z_T$ , is given by:

$$Z_T = Z_1 Z_2 Z_1 + Z_2$$

$$= 2449326.75 \angle -171.72^\circ + 210 - 3308.188j$$

$$= 2449326.75 \angle -171.72^\circ + 3314.85 \angle -86.37^\circ$$

$$= 738.9 \angle -85.35^\circ$$

This last line in rectangular form is  $Z_T = 59.9 - 736.5j \Omega$

Now:

$$I_T = V_T Z_T = 150 \angle 0^\circ / 738.9 \angle -85.35^\circ = 0.203 \angle 85.35^\circ$$

136. Three single phase 167 KVA, 14400/24940, Y-240/480 Volts transformers are connected delta-delta to supply an assorted load of 400 KW at 0.80 p.f lagging . If one transformer is taken out for repair:

- a. Determine by how much kvA each of the remaining transformer will be overloaded.

Solution:

$$a. \frac{500 \text{ KVA}}{\sqrt{3}} = 288.675 \text{ KVA}$$

$$288.675 - 167 = 121.675 \text{ KVA}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

137. A three phase, 3 wire transmission line has an impedance per wire of  $3+j7$  ohms, the receiving end load is 215 KW, 0.65 pf lagging with the line voltage of 11,200 V. Determine the kVAR of the capacitor to be connected at the receiving end to make the pf at that end to 0.8 lagging.

SOLUTION :

$$\theta_l = \cos^{-1} 0.65 = 49.458 \text{ degree}$$

$$\theta_t = \cos^{-1} 0.8 = 36.869 \text{ degree}$$

$$Q_L = P_L \tan \theta = 215 \tan 49.458 \text{ degree} = 251.359 \text{ KVAR}$$

$$Q_T = 215 \tan 36.869 \text{ degree} = 161.245 \text{ kVAR}$$

$$Q_C = 251.359 - 161.245$$

$$Q_C = 90.114 \text{ KVAR}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

138. The input to an induction motor from a 13 kV, 60 Hz line is 1000kVA, at 0.8 pf lagging. A capacitor is placed in parallel with the motor to improve the pf. Calculate the capacitance required raising the power factor to 0.9 leading.

SOLUTION:

$$\theta_L = \cos^{-1} (0.8) = 36.869$$

$$\theta_T = \cos^{-1} (0.9) = 25.84$$

$$P_L = 1000 (0.8) = 800 \text{ W}$$

$$Q_C = Q_L + Q_T$$

$$= 987.4 \text{ VAR}$$

$$X_C = \frac{230^2}{987.4} = 53.575 \text{ ohms}$$

$$C = \frac{1}{2\pi(60)(53.575)}$$

$$= 49.5 \text{ } \mu\text{F}$$

$$C \approx 50$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

139. A load of 10,000 kVA, 80 percent pf lagging is connected to a 13,200 V line. How much capacitive reactive power is needed to correct the power factor to 0.97 lagging?

SOLUTION:

$$\theta_i = \cos^{-1} 0.82 = 34.915 \text{ degree}$$

$$\theta_t = \cos^{-1} 0.9 = 25.84 \text{ degree}$$

$$P_L = S_L \text{ pf} = (998.4)(0.82) = 818.688 \text{ kW}$$

$$Q_T = (818.688)(\tan 34.915 \text{ degree} - \tan 25.84 \text{ degree})$$

$$Q_T = 175 \text{ kVAR}$$

140. An induction motor load of 1500 kW consists of several units in parallel, operating at an average power factor of 0.80 lagging. In order to improve the power factor, a portion of the induction motor loads is to be replaced by a synchronous motor, operating at the same efficiency as the induction motors and at a power factor of 0.7 leading. Find the kVA rating of the synchronous motor required bringing the power factor of the total load to 0.9 lagging. Assume the induction motor load, which has to be replaced, operates at the same pf as the induction motor group.

$$\theta_L = \cos^{-1} 0.8 = 36.869^\circ$$

$$S_L = 1500 - j1500 \tan 36.869 = 1500 - j1124.96$$

$$\theta_{\text{syn}} = \cos^{-1} 0.7 = 45.573^\circ$$

$$S_{\text{syn}} = P + jP \tan 45.573 = P + j1.02P$$

$$S_{\text{ind}} = P - jP \tan 36.869 = P - j0.75P$$

$$\theta_{\text{new}} = \cos^{-1} 0.9 = 25.84^\circ$$

$$S_{\text{new}} = 1500 - j1500 \tan 25.84 = 1500 - j726.42$$

$$S_{\text{new}} = S_L + S_{\text{Syn}} - S_{\text{ind}}$$

$$1500 - j726.42 = 1500 - j1124.96 + P + j1.02P - (P - j0.75P)$$

Equate coefficients of j:

$$-726.42 = -1124.96 + 1.02P + 0.75P$$

$$P = 225.164 \text{ kW}$$

$$S_{\text{syn}} = P / \text{pf} = 225 / 0.7 = 321.66$$

$$S_{\text{syn}} \approx 322 \text{ kVA}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

141. A single phase induction motor is rated 5 hp, 75 percent power factor and 220 volts. What approximate size of the capacitor is necessary to raise the power factor to about 95 percent?

SOLUTION:

$$\theta_i = \cos^{-1} 0.75 = 41.41 \text{ degree}$$

$$\theta_t = \cos^{-1} 0.95 = 18.195 \text{ degree}$$

$$P_L = 5(0.746) = 3.73 \text{ kW}$$

$$Q_L = 3.73 \tan 41.41 \text{ degree} = 3.289 \text{ kVAR}$$

$$Q_T = 3.73 \tan 18.195 \text{ degree} = 1.226 \text{ kVAR}$$

$$Q_C = 3.289 - 1.226 = 2.063$$

$$Q_C = 2 \text{ kVAR}$$

142. A 3-phase , 3 wire, short transmission line has a resistance of 3 ohms and a reactance of 8 ohms per wire. At the receiving end, a balanced 3-phase load draws a line current of 45 A, at 11200 V line to line, 0.90 power factor lagging. Assuming the receiving end voltage is maintained at 11,200 V, solve the size in kVAR of capacitors needed to raise the power factor at the receiving end to 0.8 leading.

SOLUTION :

$$P_R = \sqrt{3} EI \text{pf}$$

$$P_R = \sqrt{3} (11,200)(45)(0.8)$$

$$= 698.362 \text{ KW}$$

$$\theta = \cos^{-1} 0.90 = 25.84 \text{ lagging}$$

$$\theta_t = \cos^{-1} 0.8 = 36.869 \text{ degree}$$

$$Q_C = Q_R + Q_T$$

$$= 698.362 \tan 25.84 \text{ degree} + 698.362 \tan 36.869 \text{ degree}$$

$$Q_C = 861.957 \text{ kVAR}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

143. A 300 Kva transformer bank will serve a load expected to draw 122 KW At 0.80 lagging power factor. Solve for the size of the capacitor bank with needed to be acted in order to prevent overloading of the transformer bank

SOLUTION:

$$\theta_1 = \cos^{-1} 0.8 = 36.87 \text{ degree}$$

$$Q_T = \sqrt{S^2 - P^2} = \sqrt{300^2 - 122^2}$$

$$= 274.07 \text{ Kvar}$$

$$Q_C = Q_L - Q_T$$

$$= P_L \tan \theta - Q_T = 122 \tan 36.869 \text{ degree} - 274.07$$

$$Q_C = 182.57 \text{ kVAR}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

144. Three single phase 167 KVA, 14400/24940, Y-240/480 Volts transformers are connected delta-delta to supply an assorted load of 400 KW at 0.80 p.f lagging . If one transformer is taken out for repair:

- a. If load of 120 HP ,0.746 p.f lagging and 85% efficiency is removed, find the apparent power and power factor of the remaining load system.

a.  $P_i = 400 \text{ kW}$

$S = 500 \text{ KVA}$

$36.87^\circ$

$\sin \phi = 300 \text{ KVAR}$

$R = 500 \text{ KVA } \phi$

$P_i = \frac{P_o}{\text{eff}}$

$\phi = \frac{120 \text{ HP} \frac{0.746 \text{ KW}}{\text{HP}}}{0.85}$

$\phi = 105,318 \text{ KW}$

$\theta = \cos^{-1} 0.746$

$\theta = 41.755^\circ$

$R = 105,318 \tan 41.755^\circ = 94,016 \text{ ind. KVAR}$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

145. A short, 3 phase, 3 wire transmission line has a receiving end voltage of 4160 V phase neutral and serving a balanced 3 phase load of 998, 400 volt-amperes at 0.82 p.f lagging . At the receiving end the voltage is 4600V, phase to Neutral and the p.f is 0.77 . solve for the size in kVAR of a capacitor needed to improve the receiving end pf to 0.9 lagging maintaining 4160V.

SOLUTION:

$$\theta_L = \frac{1}{\cos} (0.82) = 34.915^\circ$$

$$\theta_T = \frac{1}{\cos} (0.9) = 25.84^\circ$$

$$P_L = (998.4) (0.82) = 818.688 \text{ kW}$$

$$Q_T = Q_L - Q_C$$

$$= (818.688) (\tan 34.915 - \tan 25.84)$$

$$= 175 \text{ kVAR}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

146. A plant has a load of 290kilo watt with an average power factor of 70 %. The owner request you to correct the power factor to reduce its power consumption. How much capacitor kVAR is required to increase the powerfactor to 90%?

SOLUTION:

$$\theta_L = \frac{1}{\cos} (0.7) = 45.57^\circ$$

$$\theta_t = \frac{1}{\cos} (0.9) = 25.84^\circ$$

$$Q_c = Q_L - Q_T$$

$$= 290 \tan 45.57^\circ - 290 \tan 25.84^\circ$$

$$= 155.39 \text{ kVAR}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

147. A 150 Kva transformer bank will serve a load expected to draw 135 KW At 0.80 lagging power factor. Solve for the size of the capacitor bank with needed to be acted in order to prevent overloading of the transformer bank

SOLUTION:

$$\theta_1 = \cos^{-1} 0.8 = 36.87 \text{ degree}$$

$$Q_T = \sqrt{S^2 - P^2} = \sqrt{150^2 - 135^2}$$

$$= 65.38 \text{ Kvar}$$

$$Q_C = Q_L - Q_T$$

$$= P_L \tan \theta - Q_T = 135 \tan 36.869 \text{ degree} - 65.38$$

$$Q_C = 35.866 \text{ kVAR}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

148. A current of 12A and a power factor of 0.6 lagging is taken from a single phase 220 V supply. The reactive power of the system is :

SOLUTION :

$$\theta = \cos^{-1} 0.6 = 53.13 \text{ degree}$$

$$Q = EI \sin \theta$$

$$Q = (220 \times 12) \sin 53.13 \text{ degree}$$

$$Q = 2112 \text{ VARS}$$

Group IV

June 4,2013

EE 3303

Engr.Kenneth F. Fajilan

149. An inductive reactance of 10 ohms is connected in parallel with a capacitive reactance of 20 ohms. If the combination is connected in series with a 10 ohms resistance. Solve for the equivalent power factor of the combination.

SOLUTION :

$$Z_1 = 10 + \frac{(J 10)(-J 20)}{(J 10 + J 20)}$$

$$Z_1 = 10 + \frac{-j^2(200)}{-j 30} = 10 + j6.67$$

$$Z_1 = 10 - 6.67i$$

$$\text{Pf} = \cos 33.70$$

$$\text{Pf} = 0.83 \text{ lagging}$$

Group IV

June 4, 2013

EE 3303

Engr. Kenneth F. Fajilan

150. Given three impedances:  $Z_1 = 10+j2$ ,  $Z_2 = 2+j5$ ,  $Z_3 = 3-j2$ . Impedance  $Z_2$  and  $Z_3$  are connected in parallel and the combination is connected in series with impedance  $Z_1$ , across 120 V single phase 60 Hz source. Find the total power drawn by the impedances.

SOLUTION:

$$Z_1 = 10+j2$$

$$Z_2 = 2+j5$$

$$Z_3 = 3-j2$$

$$Z_T = 10 + \frac{10+2j(3-j2)}{j}$$

$$= 10+2.62-1.08j$$

$$P = \frac{120^2}{12.62} \cos (4.89 \text{ degree})$$

$$P = 1136.89 \text{ watts}$$









Group IV	June
EE 3303	Engr.Kenneth F. Fajilan

Group IV	June 4,2013
EE 3303	Engr.Kenneth F. Fajilan





